

# Computer System Architecture

**Ms. Yuzana Hlaing**

**M.E(IT), Ph.D. Candidate(thesis)**

**Lecturer**

**Computer Engineering and Information Technology Dept.  
Yangon Technological University**

# Course Schedule

Periods	Lectures
Week-1	Introduction to Computer System Architecture
Week-2	Data Presentations
<b>Week-3</b>	<b>Register Transfer and Microoperations</b>
Week-4	Basic Computer Organization and Design
Week-5	Programming the Basic Computer
Week-6	Microprogrammed Control
Week-7	Central Processing Unit
Week-8	Pipeline and Vector Processing
Week-9	Computer Arithmetic
Week-10	Input-Output Organization
Week-11	Memory Organization
Week-12	Multiprocessors

# Lecture-3



## Register Transfer and Microoperations

# Lecture-3

## Register Transfer and Microoperations

- Register Transfer Language
- Register transfer
- Bus and Memory Transfers
- Arithmetic Microoperations
- Logic Microoperations
- Shift Microoperations
- Arithmetic Logic Shift Unit

# Register Transfer Language

# Register Transfer Language

- A **digital system** is a interconnection of digital hardware modules that accomplish a specific information-processing task.
- The operations executed on data stored in registers are called **microoperations**.
- The symbolic notation used to describe the microoperation transfers among registers is called **register transfer language**.
- The **internal hardware organization** of a digital computer is defined by specifying
  1. The set of registers it contains and their function.
  2. The sequence of microoperations performed on the binary information stored in the registers.
  3. The control that initiates the sequence of microoperations.

# Register Transfer

# Register Transfer

- **Register transfer** implies the availability of hardware logic circuits that can perform a stated microoperation and transfer the result of the operation to the same or another register.
- Different types of register are defined as follows;
  - Memory Address Register (MAR)
  - Instruction Register (IR)
  - Program Counter (PC)
  - Processor register (R1, R2, etc)

 



Fig: Block diagram of a register

\*\*\* **Example:** Represent the following statement by register transfer statement and show the block diagram with its timing diagram for this statement.


If ( $P = 1$ ) then ( $R2 \leftarrow R1$ )

Sol:

**P:  $R2 \leftarrow R1$**

 

(a) Block diagram

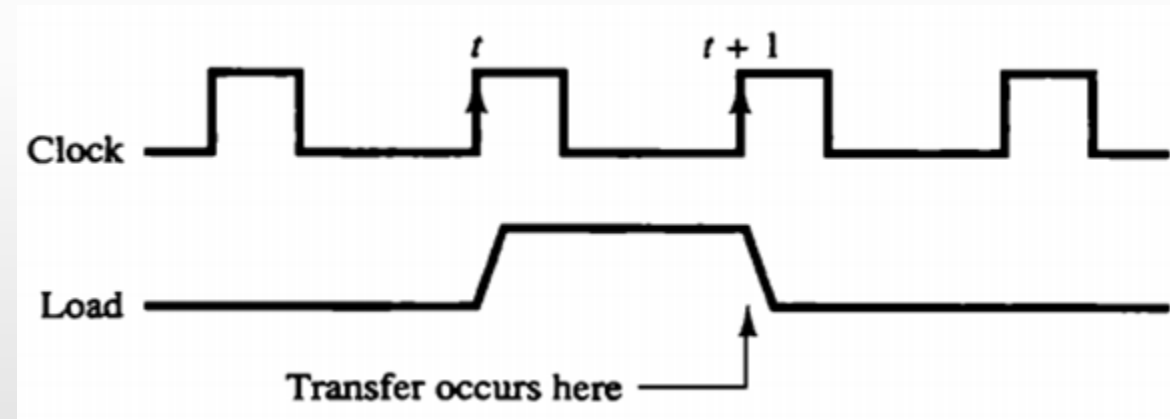

(b) Timing Diagram

\*\*\* **Example:** Represent the following statement by register transfer statement and show the block diagram for this statement.

If ( $y = 1$  and  $T = 1$ ) then ( $R2 \leftarrow R1, R1 \leftarrow R2$ )

Sol:

**$yT: R2 \leftarrow R1, R1 \leftarrow R2$**

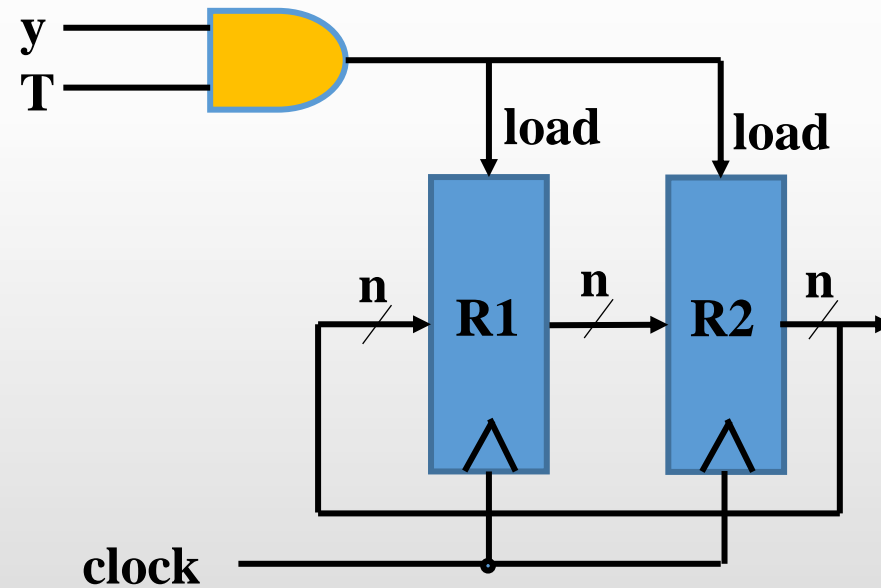


Fig: Logic diagram

# Bus and Memory Transfers

# Bus Transfer

- The content of register C is **placed** on the bus, and the content of the bus is **loaded** into register **R1** by activating its load control input.

$$\text{Bus} \leftarrow \text{C}, \text{R1} \leftarrow \text{Bus}$$

- If the bus is known to exist in the system, it may be convenient just to show the **direct transfer**.

$$\text{R1} \leftarrow \text{C}$$

- For example, the bus system for **4-bit** four registers by using 1-bit multiplexers with its function table are as shown in the following.
- For 4-bits four registers,
  - **Number of multiplexers = Number of bits in register**
  - **Number of input lines in multiplexer = Number of registers**

$S_0$	$S_1$	Register Selected
0	0	A
0	1	B
1	0	C
1	1	D

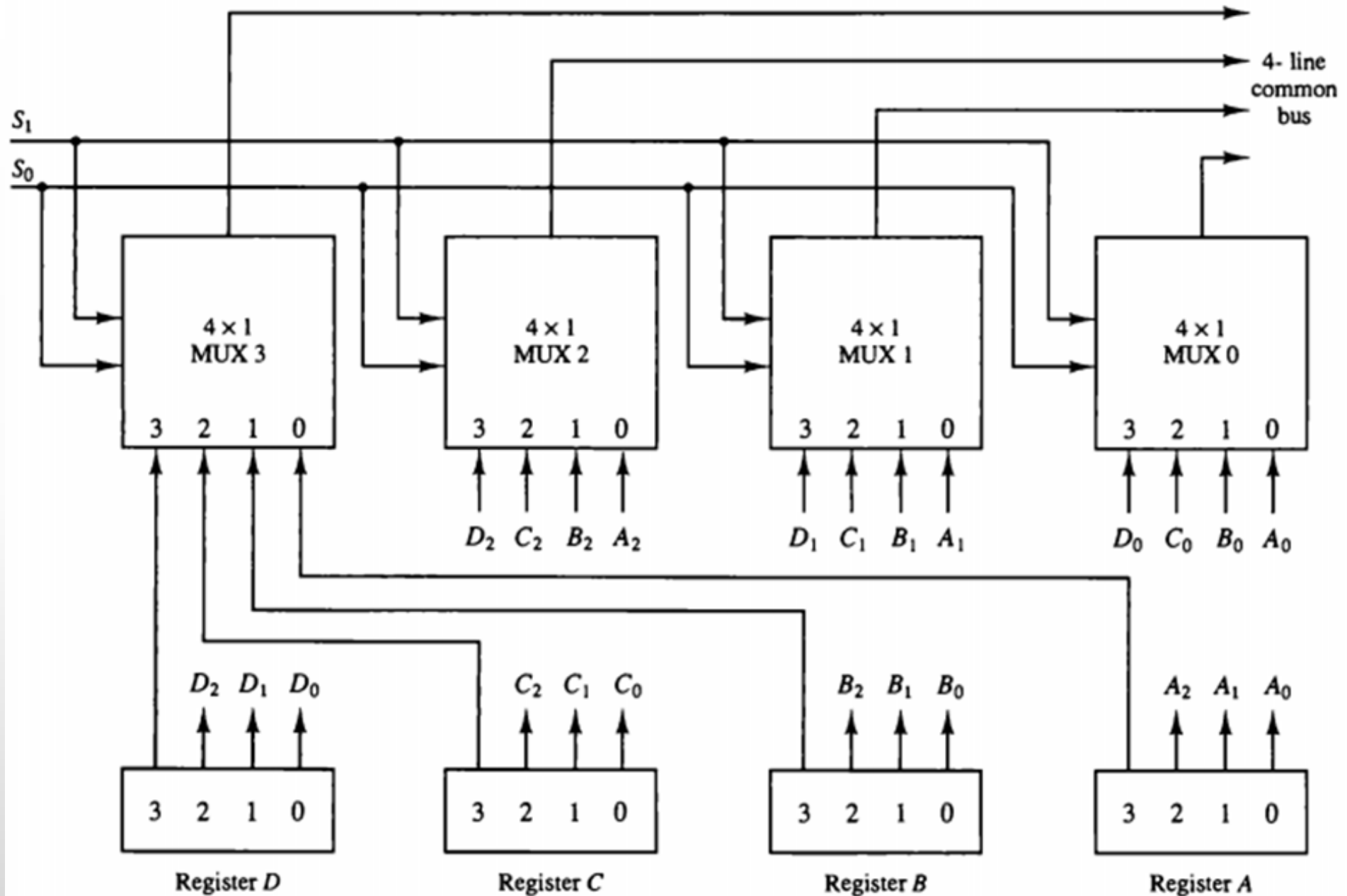


Fig: Bus system for 4-bit four registers

\*\*\* **Example:** Design the circuit for register transfers that data of 8-bit four registers R1, R2, R3 and R4 are connected to 8-bit 4x1 multiplexers to the inputs of fifth register R5. The required transfers are dictated by four timing variables  $T_0$  through  $T_3$  as follows.

$T_0$ :  $R5 \leftarrow R1$

$T_1$ :  $R5 \leftarrow R2$

$T_2$ :  $R5 \leftarrow R3$

$T_3$ :  $R5 \leftarrow R4$

Sol:

$T_3$	$T_2$	$T_1$	$T_0$	$S_1$	$S_0$	Y	Load
0	0	0	0	x	x	0	0
0	0	0	1	0	0	R1	1
0	0	1	0	0	1	R2	1
0	1	0	0	1	0	R3	1
1	0	0	0	1	1	R4	1

$$S_1 = T_2 + T_3$$

$$S_0 = T_1 + T_3$$

$$\text{Load} = T_0 + T_1 + T_2 + T_3$$


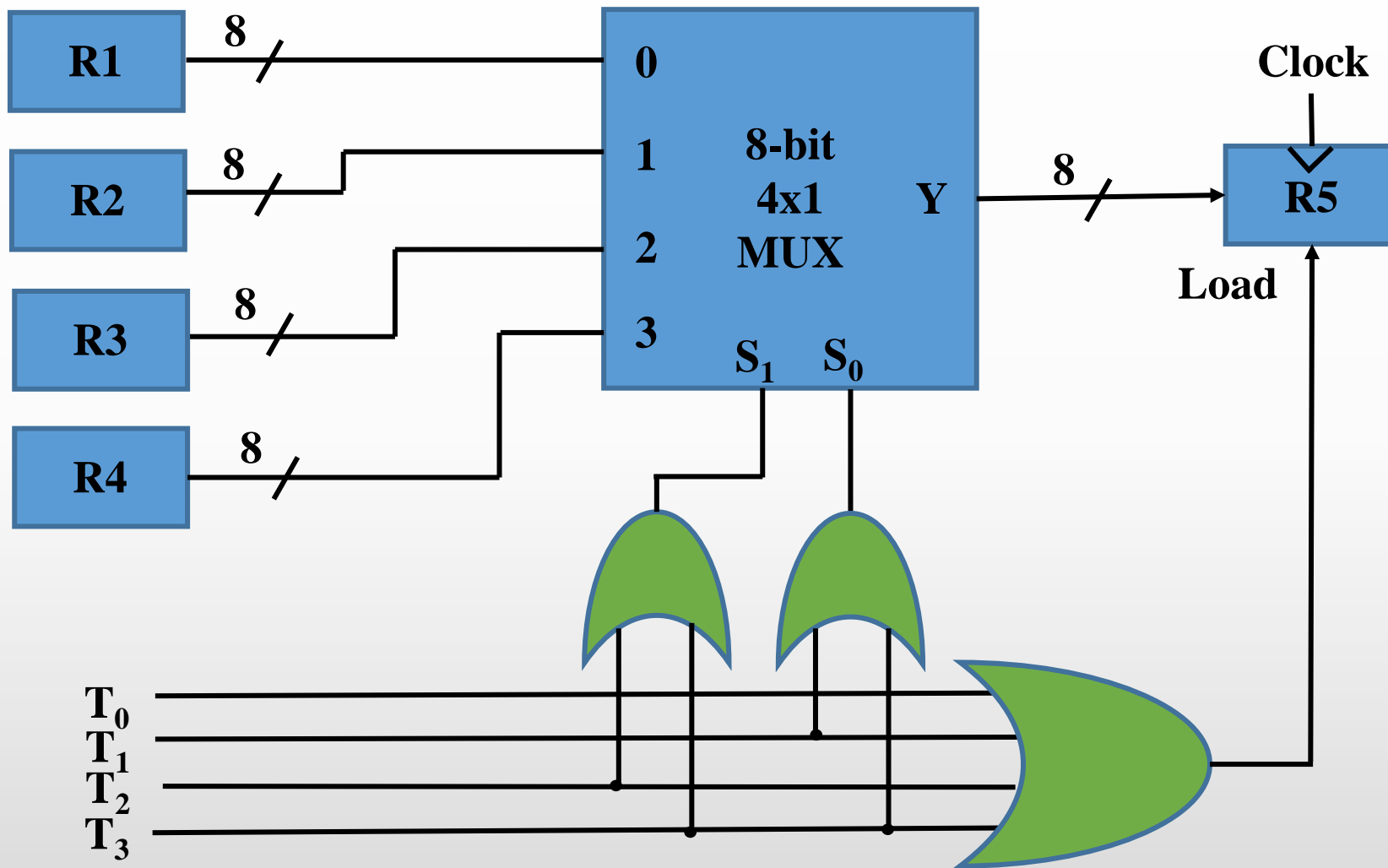


Fig: Block diagram for register transfers
 
## Three-State Bus Buffers

- A bus system can be constructed with **three-state gates** instead of multiplexers.
- A three-state gate is a digital circuit that exhibits three states.
- Two of the states are signals equivalent to logic **1** and **0** as in conventional gate.
- The third state is a **high-impedance** state that behaves like an open circuit.
- The three-state gates may perform any conventional logic such as **AND** or **NAND**.



Graphic symbols for three-state buffer

- A bus line for 1-bit four registers can be designed by using decoder and three state-buffers.

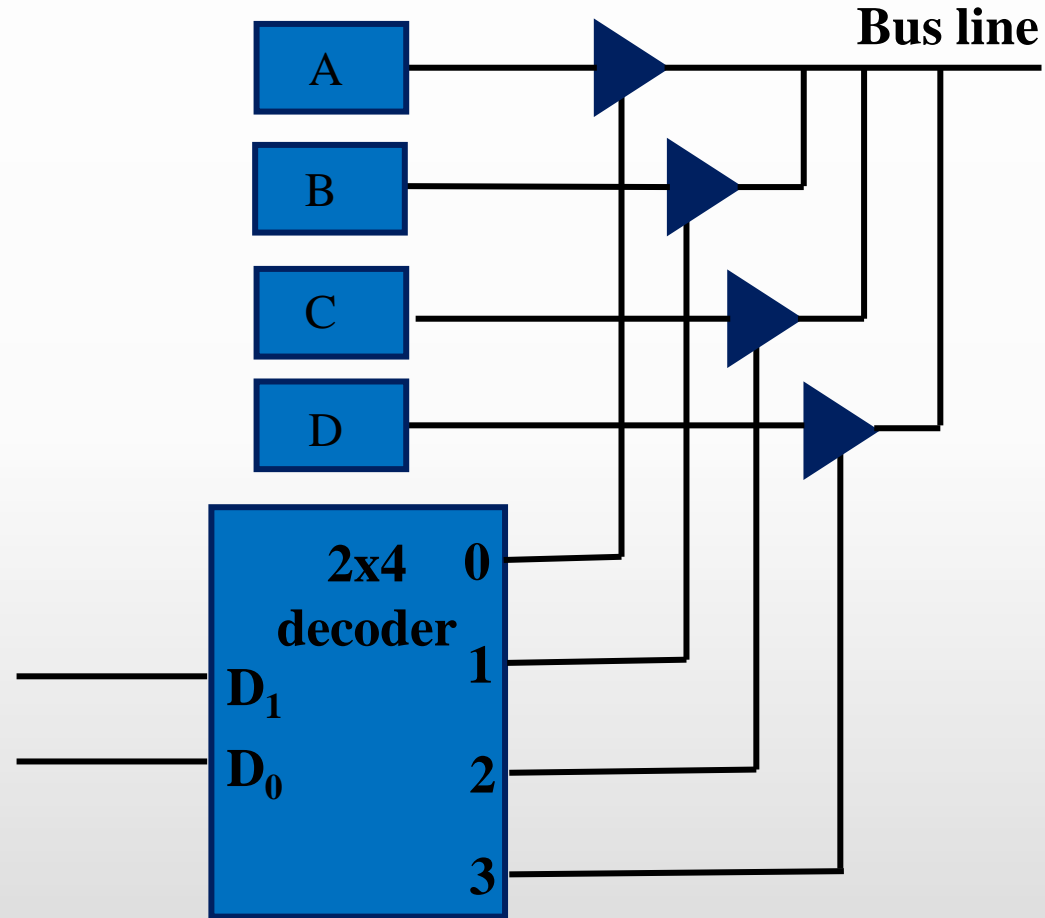


Fig: Bus line for 1-bit four registers with three state-buffers

# Memory Transfer

- The transfer of information from a memory word to the outside environment is called a **read operation**.

**Read:  $DR \leftarrow M[AR]$**

- The transfer of new information to be stored into the memory is called a **write operation**.

**Write:  $M[AR] \leftarrow DR$**

- Symbolic designation of arithmetic microoperations are
  - $R3 \leftarrow R1 + R2$
  - $R3 \leftarrow \underline{R1} - R2$
  - $R2 \leftarrow \underline{R2}$
  - $R2 \leftarrow R2 + \underline{1}$
  - $R3 \leftarrow R1 + R2 + 1$
  - $R1 \leftarrow R1 + 1$
  - $R1 \leftarrow R1 - 1$

# Arithmetic Microoperations

# Arithmetic Microoperations

- The most basic arithmetic microoperations for basic computer are described in the following table.

<b>Symbolic designation</b>	<b>Description</b>
$R3 \leftarrow R1 + R2$	Contents of R1 plus R2 transferred to R3
$R3 \leftarrow R1 - R2$	Contents of R1 minus R2 transferred to R3
$R2 \leftarrow R2'$	Complement the content of R2 (1's complement)
$R2 = R2' + 1$	2's complement the content of R2 (negate)
$R3 \leftarrow R1 + R2' + 1$	R1 plus 2's complement of R2 transferred to R3 (subtract)
$R1 \leftarrow R1 + 1$	Increment the content of R1 by one
$R1 \leftarrow R1 - 1$	Decrement the content of R1 by one

# Binary Adder

- An  $n$ -bit binary adder requires  $n$  full-adder.
- A 4-bit binary adder is designed by combining 1-bit full adders.

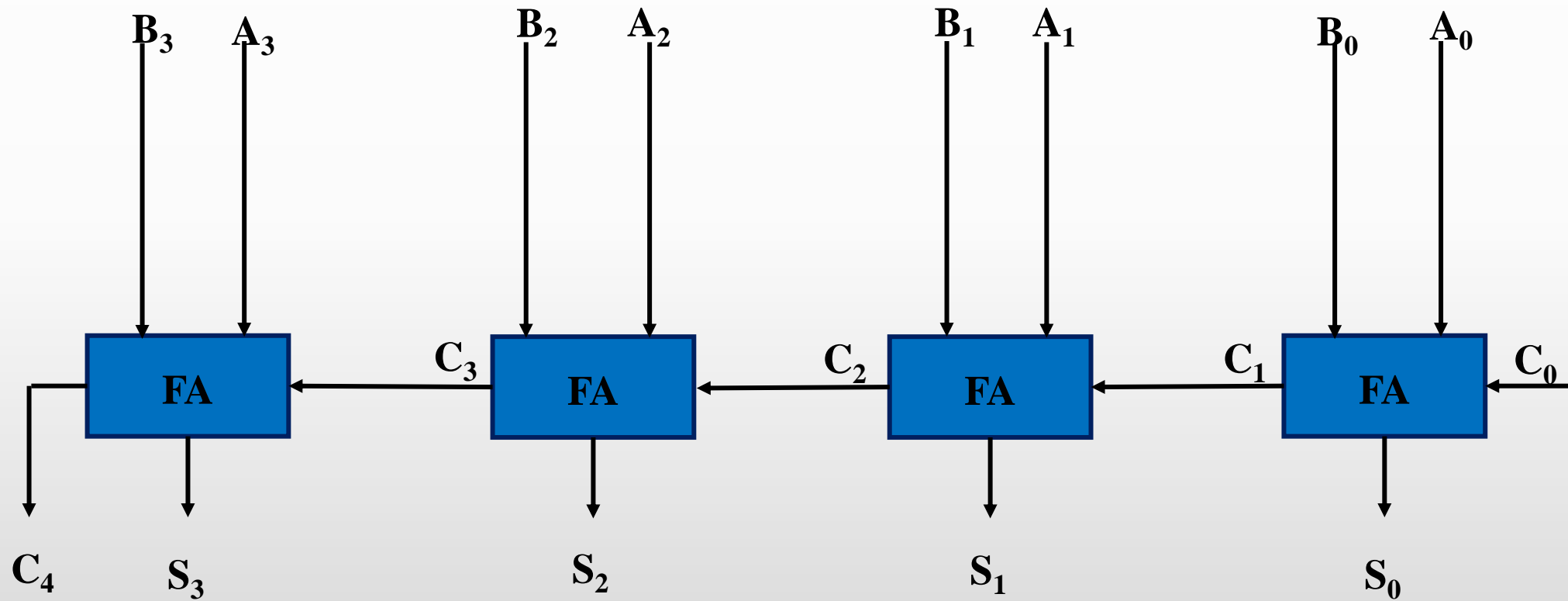


Fig: Block diagram of 4-bit binary adder

## Binary Adder-Subtractor

- The subtraction of binary numbers can be computed by means of complements.
- The **4-bit binary adder-subtractor** is designed to compute  $(A+B)$  and  $(A-B)$  using 1-bit full adders and required gates.
- The addition and subtraction operations can be combined into one common circuit by including an **exclusive-OR** gate with each **full-adder**.
- The mode input **M** controls the operation.
- When **M = 0**, the circuit is an adder  $(A+B)$ .
- When **M = 1**, the circuit becomes a subtractor  $(A-B)$ .
- Each exclusive-OR gate **receives** input **M** and one of the inputs of **B**.

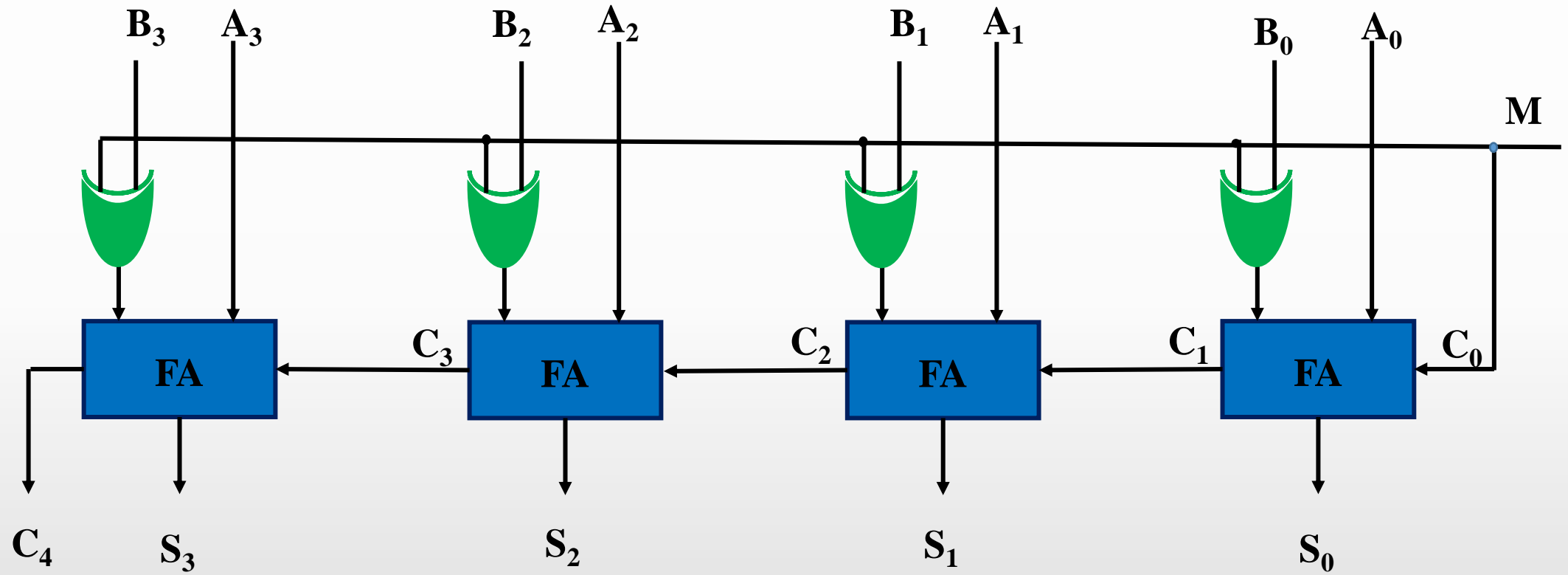


Fig: Block diagram of binary adder-subtractor

For example,

$$A=1100 \Rightarrow 12$$

$$B=1001 \Rightarrow 9$$

$$1\text{'com for } B \Rightarrow 0110$$

$$2\text{'com for } B \Rightarrow 0110$$

$$\begin{array}{r} + 1 \\ \hline 0111 \end{array}$$

$$\text{For } A + B \Rightarrow 1100$$

$$1001$$

$$\underline{10101} \Rightarrow 21$$

$$\text{For } A - B \Rightarrow -B = \overline{\overline{B}} + 1 = 2\text{'com for } B$$

$$\Rightarrow A + \overline{\overline{B}} + 1$$

$$\Rightarrow 1100$$

$$+ \underline{0111}$$

$$10011 \Rightarrow 3$$

# Binary Incrementer

- A **binary incrementer** operates the increment microoperation that adds one to a number in a register.

 



Fig: Block diagram of binary incrementer

# Arithmetic Circuit

- A **4-bit arithmetic circuit** can operate arithmetic microoperations with its function table.
- The basic component of an arithmetic circuit is the **parallel adder**.
- By **controlling** the data inputs to the adder, it is possible to obtain different types of arithmetic operations.
- When  $S_1S_0 = 00$ , if  $C_{in} = 0$ ,  $D = A + B$ ,                      if  $C_{in} = 1$ , output  $D = A + B + 1$ .
- When  $S_1S_0 = 01$ , if  $C_{in} = 0$ ,  $D = A - B - 1$ ,                      if  $C_{in} = 1$ , output  $D = A - B$ .
- When  $S_1S_0 = 10$ , if  $C_{in} = 0$ ,  $D = A + 0 = A$ ,                      if  $C_{in} = 1$ , output  $D = A + 1$ .
- When  $S_1S_0 = 11$ , if  $C_{in} = 0$ ,  $D = A - 1$ ,                      if  $C_{in} = 1$ , output  $D = A - 1 + 1 = A$  .

## Arithmetic Circuit Function table

Select			Input	Output	Microoperations
$S_1$	$S_0$	$C_{in}$			
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	$\overline{B}$	$D = A + \overline{B}$	Subtract with borrow
0	1	1	$\overline{B}$	$D = A + \overline{B} + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

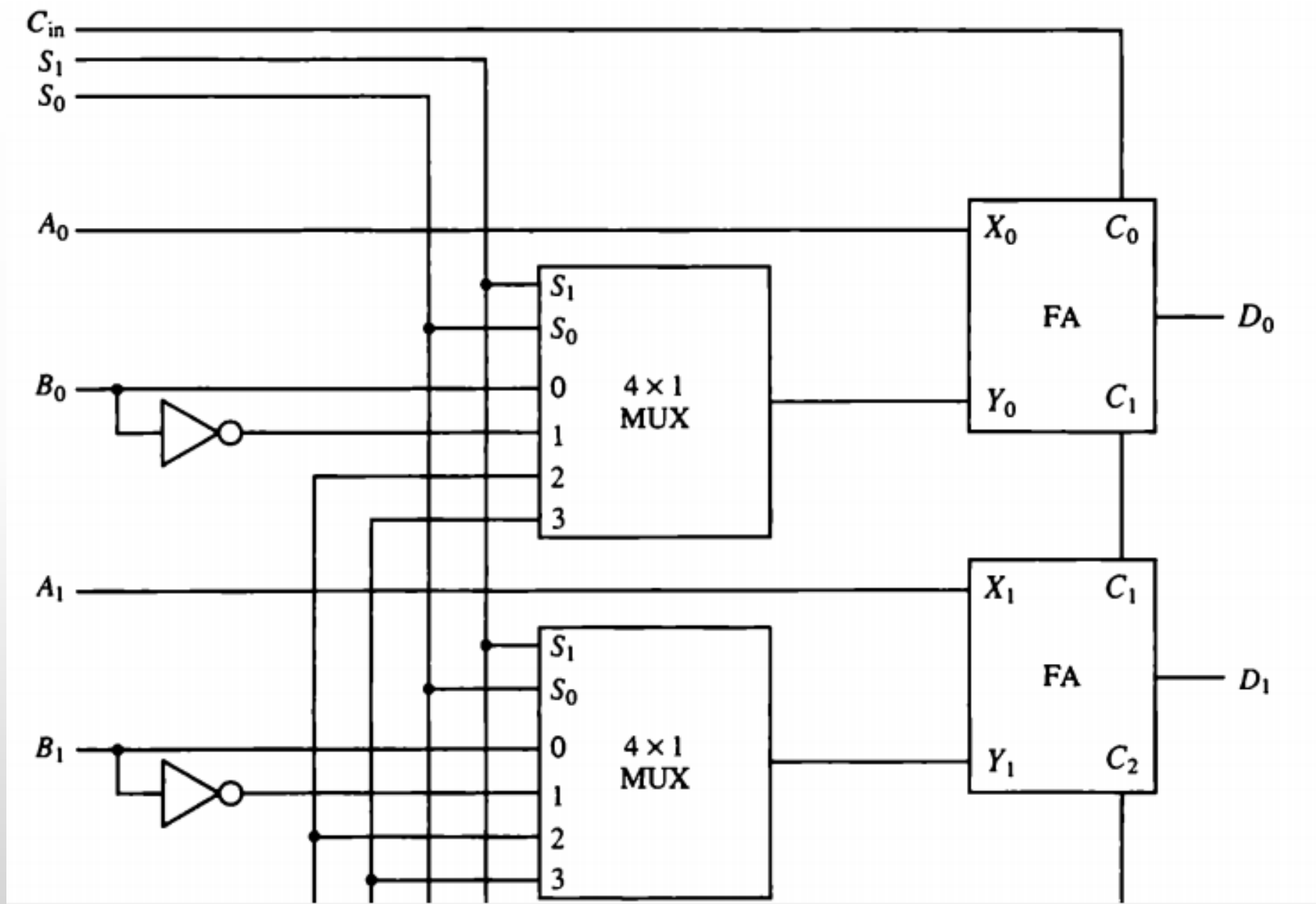

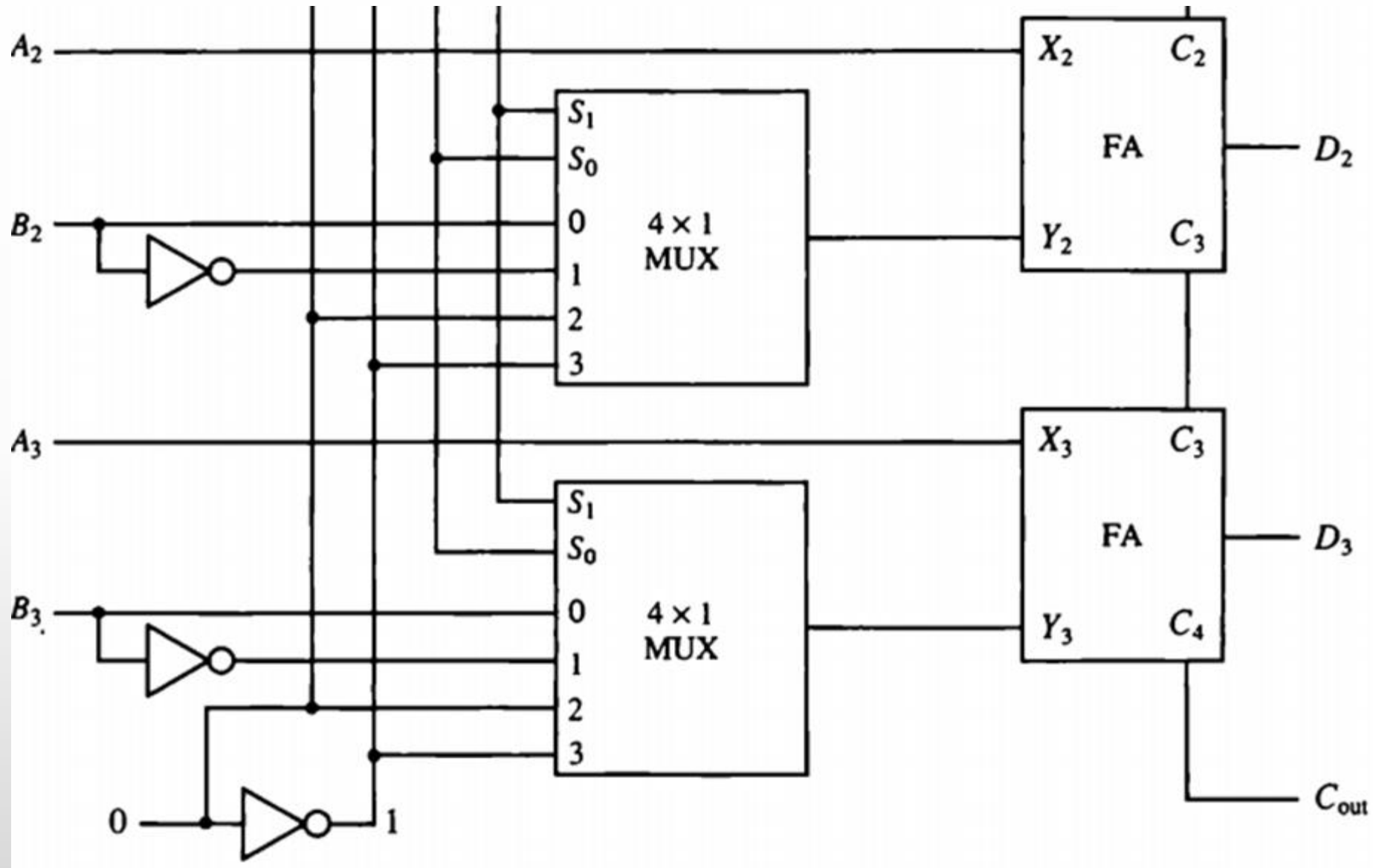


Fig: Block diagram of 4-bit arithmetic circuit.

# Logic Microoperations

# Logic Microoperations

- Logic microoperations specify **binary operations** for strings of bits stored in registers.
- For example, exclusive-OR microoperation is performed as follows,

$$P: R1 \leftarrow R1 \oplus R2$$

1010 Content of R1

1100 Content of R2

---

0110 Content of R1 after P = 1

# Sixteen Logic Microoperations


Boolean Function	Microoperation	Name
$F_0 = 0$	$F \leftarrow 0$	Clear
$F_1 = xy$	$F \leftarrow A \wedge B$	AND
$F_2 = xy'$	$F \leftarrow A \wedge \overline{B}$	
$F_3 = x$	$F \leftarrow A$	Transfer A
$F_4 = x'y$	$F \leftarrow \overline{A} \wedge B$	
$F_5 = y$	$F \leftarrow B$	Transfer B
$F_6 = x \oplus y$	$F \leftarrow A \oplus B$	Exclusive-OR
$F_7 = x + y$	$F \leftarrow A \vee B$	OR
$F_8 = (x + y)'$	$F \leftarrow \overline{A \vee B}$	NOR
$F_9 = (x \oplus y)'$	$F \leftarrow A \oplus B$	Exclusive-NOR
$F_{10} = y'$	$F \leftarrow \overline{B}$	Complement B
$F_{11} = x + y'$	$F \leftarrow A \vee \overline{B}$	
$F_{12} = x'$	$F \leftarrow \overline{A}$	Complement A
$F_{13} = x' + y$	$F \leftarrow \overline{A} \vee B$	
$F_{14} = (xy)'$	$F \leftarrow \overline{A \wedge B}$	NAND
$F_{15} = 1$	$F \leftarrow \text{all 1's}$	Set to all 1's

\*\*\***Example:** Design a logic circuit that can operate 4 logic microoperations (AND, OR, exclusive-OR, NOT) with its function table.

Sol:

$S_1$	$S_0$	Output	Operation
0	0	$E=A \wedge B$	AND
0	1	$E=A \vee B$	OR
1	0	$E=\underline{A} \oplus B$	XOR
1	1	$E=\underline{A}$	Complement

Function Table

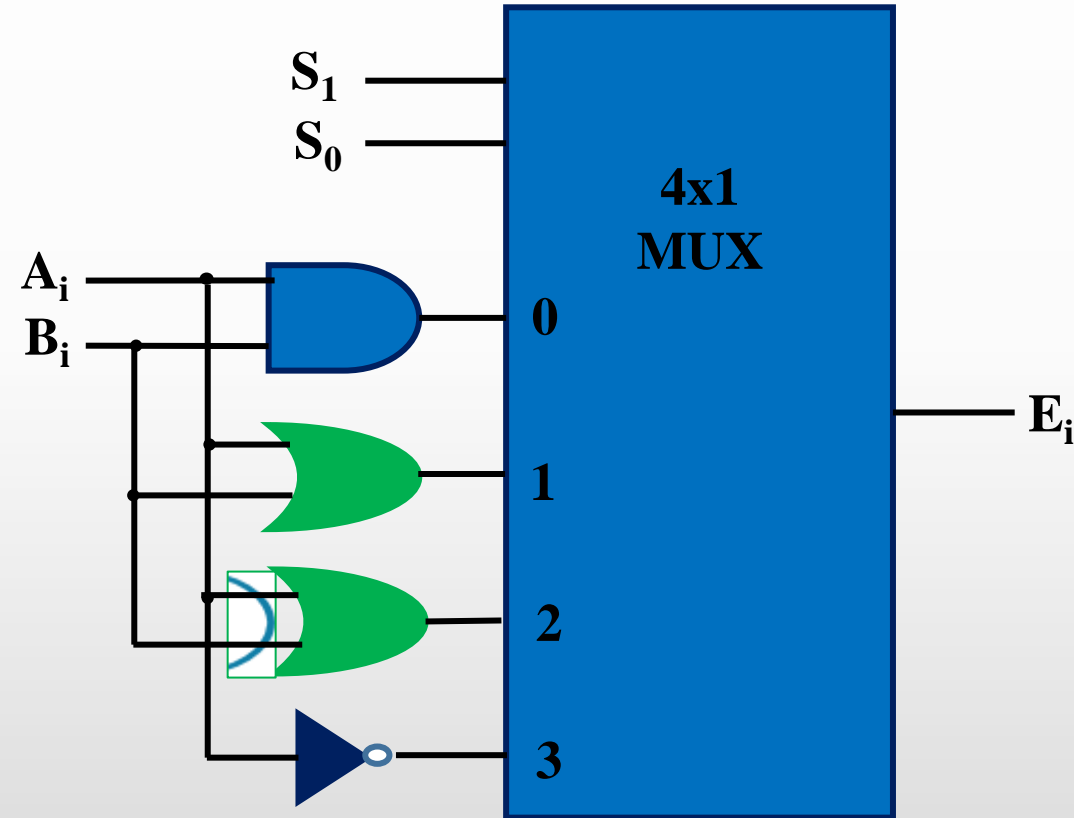


Logic Diagram

\*\*\***Example:** Design a logic circuit that can operate 4 logic microoperations (EX-OR, EX-NOR, NOR, NAND) with its function table.

Sol:

$S_1$	$S_0$	Output	Operation
0	0	$E = A \oplus B$	XOR
0	1	$E = \overline{A \oplus B}$	X-NOR
1	0	$E = \overline{A \vee B}$	NOR
1	1	$E = \overline{A \wedge B}$	NAND

Function Table

 

Logic Diagram

The following logic microoperations are used in digital system.

### Selective-set operation

- Selective-set operation set to 1 the bits in A only where there are corresponding 1's in B.

1010	A before
<u>1100</u>	B (logic operand)
1110	A after

### Selective-complement operation

- Selective-complement operation complements bits in A only where there are 1's in B.

1010	A before
<u>1100</u>	B (logic operand)
0110	A after

### Selective-clear operation

- Selective-clear operation clears to 0 the bits in A only where there are corresponding 1's in B.

1010	A before
<u>1100</u>	B (logic operand)
0010	A after

## Mask operation

- The mask operation is similar to the selective-clear operation except that the bits of A are cleared only where there are corresponding 0's in B.

$$\begin{array}{r} 1010 \\ 1100 \\ \hline 1000 \end{array} \quad \begin{array}{l} \text{A before} \\ \text{B (logic operand)} \\ \text{A after masking} \end{array}$$

## Clear operation

- All 0's result if the two numbers are equal.
- The content in register B is inserted by copying the content of register A.

$$\begin{array}{r} 1010 \\ 1010 \\ \hline 0000 \end{array} \quad \begin{array}{l} \text{A} \\ \text{B} \\ \text{A} \end{array}$$

## Insert operation

The insert operation inserts a new value into a group of bits. This is done by first masking the bits and then ORing them with the required value.

```
0110 1010 A before
0000 1111 B (mask)
0000 1010 A after masking
```

```
0000 1010 A before
1001 0000 B (insert)
1001 1010 A after intersection
```

# Shift Microoperations


# Shift Microoperations

Shift microoperations are used for **serial** transfer of data. There are **three** types of shifts: logical, circular, and arithmetic.

- A **logical shift** is one that transfers 0 through the serial input. Symbols shl and shr are for logical shift-left and shift-right microoperations.
- The **circular shift** or **rotate operation** circulates the bits of the register around the two ends without loss of information.
- An **arithmetic shift** is a microoperation that shifts a signed binary number to the left or right.
  - An **arithmetic shift-left** **multiplies** a signed binary number by 2.
  - An **arithmetic shift-right** **divides** the number by 2.

# Examples of Shift Microoperations

Symbolic designation	Description
$R \leftarrow \text{shl } R$	Shift-left register R
$R \leftarrow \text{shr } R$	Shift-right register R
$R \leftarrow \text{cil } R$	Circular shift-left register R
$R \leftarrow \text{cir } R$	Circular shift-right register R
$R \leftarrow \text{ashl } R$	Arithmetic shift-left R
$R \leftarrow \text{ashr } R$	Arithmetic shift-right R

 

Sign bit

Arithmetic shift right

# Hardware Implementation of Shifter

- A 4-bit combinational circuit **shifter** can be designed by using **multiplexers** with its function table.
- A shifter with  $n$  data inputs and outputs requires  $n$  multiplexers.
- When the select line  $S = 1$ , the input data are shifted **left**.
- When the select line  $S = 0$ , the input data are shifted **right**.
- The two serial inputs can be controlled by another multiplexer to provide three possible types of shift.

Select $S$	Output			
	$H_0$	$H_1$	$H_2$	$H_3$
0	$I_R$	$A_0$	$A_1$	$A_2$
1	$A_1$	$A_2$	$A_3$	$I_L$

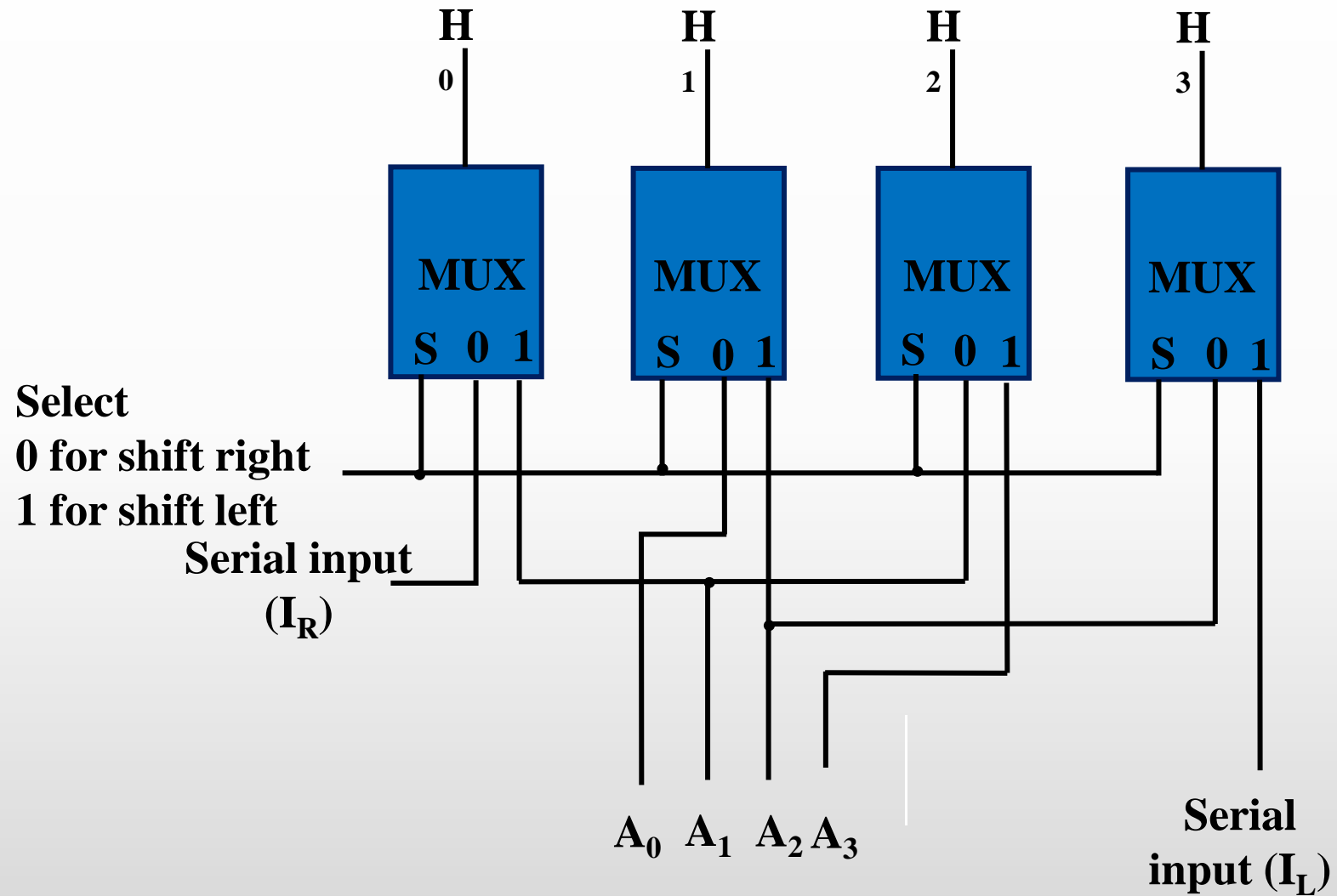


Fig: 4-bit combinational circuit shifter

# **Arithmetic Logic Shift Unit**


# Arithmetic Logic Shift Unit

- Computer systems employ a number of storage registers connected to a **common operational unit** called an arithmetic logic unit, ALU.
- The ALU performs an operation and the result of the operation is then transferred to a destination register.
- The ALU is a combinational circuit so that the entire register transfer operation from the source registers through the ALU and into the destination register can be performed **during one clock pulse period**.
- The **shift microoperations** are often performed in a **separate unit**, but sometimes the shift unit is made part of the overall ALU.

# Function Table for Arithmetic Logic Shift Unit

Operation select					Operation	Function
S <sub>3</sub>	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	C <sub>in</sub>		
0	0	0	0	0	$F = A$	Transfer A
0	0	0	0	1	$F = A + 1$	Increment A
0	0	0	1	0	$F = A + B$	Addition
0	0	0	1	1	$F = A + \overline{B} + 1$	Add with carry
0	0	1	0	0	$F = A + \overline{B}$	Subtract with borrow
0	0	1	0	1	$F = A + \overline{B} + 1$	Subtraction
0	0	1	1	0	$F = A - 1$	Decrement A
0	0	1	1	1	$F = A$	Transfer A
0	1	0	0	x	$F = A \wedge B$	AND
0	1	0	1	x	$F = A \vee B$	OR
0	1	1	0	x	$F = A \oplus B$	XOR
0	1	1	1	x	$F = \overline{A}$	Complement A
1	0	x	x	x	$F = \text{shr } A$	Shift right A into F
1	1	x	x	x	$F = \text{shl } A$	Shift left A into F

# Arithmetic Logic Shift Unit

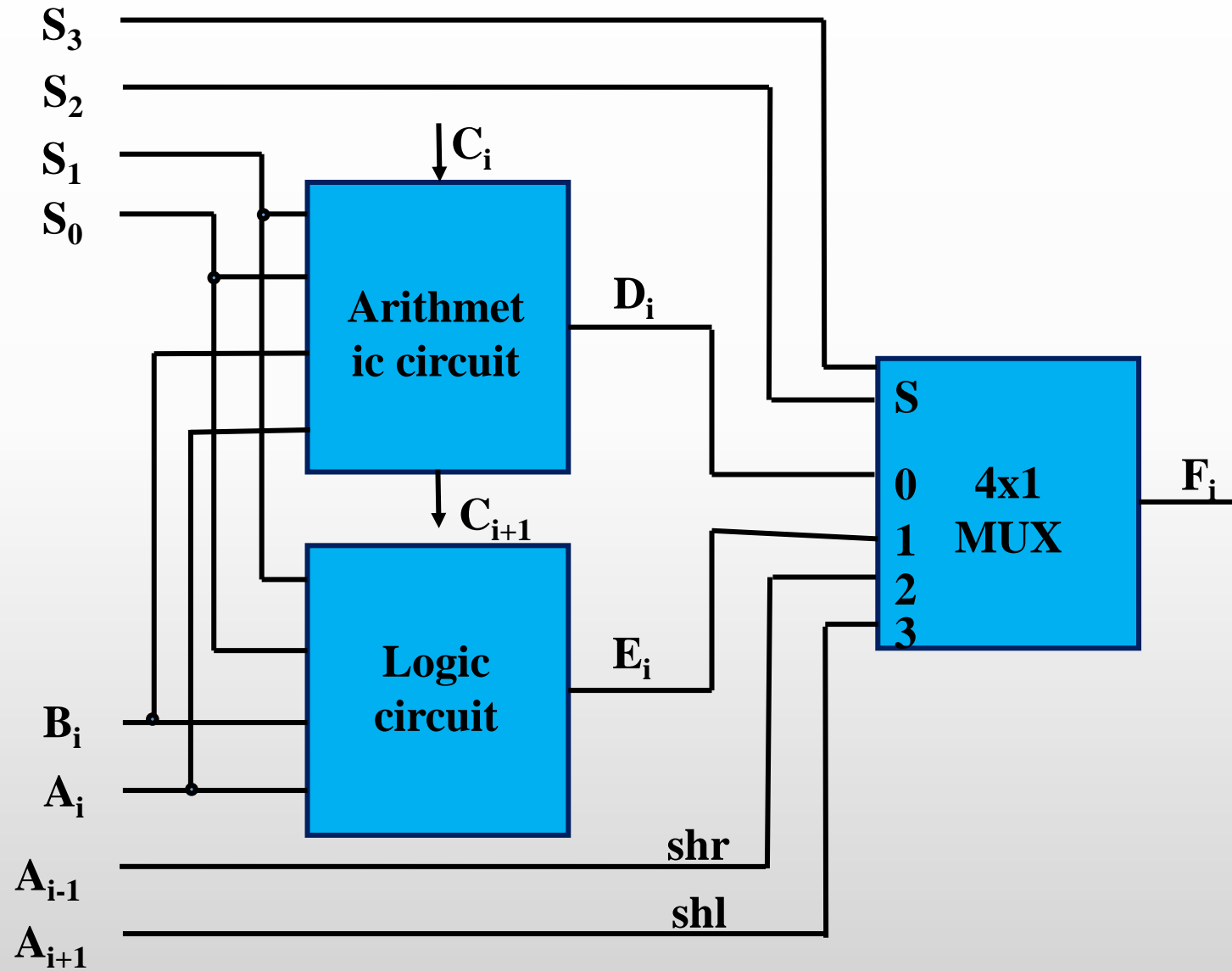


# Exercises

**Ex:1.** Draw the block diagram for the hardware that implements the following statements:

$$x + yz: \mathbf{AR} \leftarrow \mathbf{AR} + \mathbf{BR}$$

Sol:

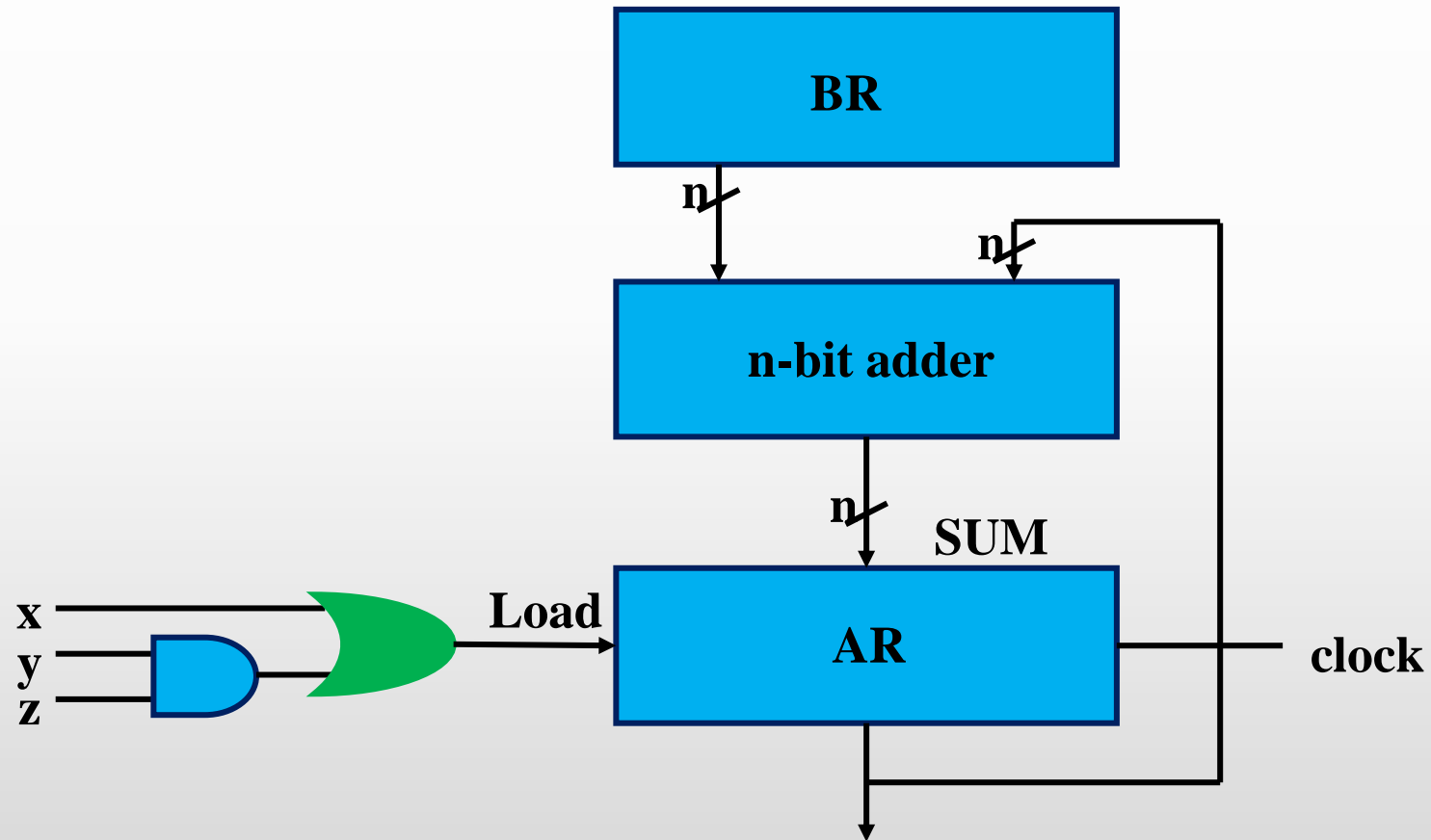

**Ex:2.** The 8-bit registers AR, BR, CR, and DR initially have the following values:  
AR = 11110010 BR = 11111111 CR = 10111001 DR = 11101010 Determine the 8-bit values in each register after the execution of the following sequence of microoperations.

- |  |                            |
|--|----------------------------|
| (a) $AR \leftarrow AR + BR$                            | Add BR to AR               |
| (b) $CR \leftarrow CR \wedge DR, BR \leftarrow BR + 1$ | AND DR to CR, increment BR |
| (c) $AR \leftarrow AR - CR$                            | Subtract CR from AR        |

Sol:

(a)

AR = 11110010

BR = 11111111 (+)

---

AR = 11110001

After calculation,

AR = 11110001 BR = 11111111 CR = 10111001 DR = 11101010

(b)

CR = 10111001

DR = 11101010 (AND)

BR = 11111111

+1

---

CR = 10101000

---

BR = 00000000

After calculation,

AR = 11110001 BR = 00000000 CR = 10101000 DR = 11101010

(d)

AR = 11110001

CR = 10101000 (-)

---

AR = 01001001

After calculation,

AR = 01001001 BR = 00000000 CR = 10101000 DR = 11101010

**Ex:3.** An 8-bit register contains the binary value 10011100. What is the register value after an arithmetic shift right? Starting from the initial number 10011100, determine the register value after an arithmetic shift left, and state whether there is an overflow. Also determine the decimal values after shifting.

Sol:

**R = 10011100 = -100**

Arithmetic shift right : **11001110 = -50**

Arithmetic shift left : **00111000**

(In arithmetic shift left, if the leftmost bit is changed, the overflow occurs and the result in register is incomplete.)

After an arithmetic shift left, overflow **occurs** because a **negative** number **changed** to **positive**.

**Ex:4.** Starting from an initial value of  $R = 11011101$ , determine the sequence of binary values in  $R$  after a logical shift-left, followed by a circular shift-right, followed by a logical shift-right and a circular shift-left.

Sol:

**$R = 11011101$**

Logical shift left : **10111010**

Circular shift right: **01011101**

Logical shift right : **00101110**

Circular shift left : **01011100**

# *Thank You*

## Lecture for Next Week



- **Basic Computer Organization and Design**
  - **Instruction Codes**
  - **Computer Registers**
  - **Computer Instructions**
  - **Timing and Control**
  - **Instruction Cycle.....**