

Computer System Architecture

Ms. Yuzana Hlaing

M.E(IT), Ph.D. Candidate(thesis)

Lecturer

**Computer Engineering and Information Technology Dept.
Yangon Technological University**

Course Information

Course Title: Computer System Architecture

Text Book: *Computer System Architecture*, International Edition, Third Edition by M. Morris Mano.

Reference: *Computer Organization and Design*, Tenth Edition by William Stallings

Course Duration: 12 weeks

Course Objectives

- To understand the **basic concepts** of the hardware operation of the logic level components in order to have the skill to design the digital circuits.
- To be able to develop the **implementation** of the computer hardware applications.
- To get the ability of **designing and programming** the advanced digital circuits to process many functions and operations.
- To support the **creative thinking** of how to improve the existing computer system in order to increase performance of this system.

Course Preface

This course deals with **computer architecture** as well as **computer organization and design**.

- **Computer organization** is concerned with how the hardware components operate and how they are connected together to form the computer system.
- **Computer design or Computer implementation** is concerned with what hardware should be used and how the parts should be connected.
- **Computer architecture** is concerned with the structure and behavior of the computer as seen by the users.

Course Schedule

Periods	Lectures
Week-1	Introduction to Computer System Architecture
Week-2	Data Presentations
Week-3	Register Transfer and Microoperations
Week-4	Basic Computer Organization and Design
Week-5	Programming the Basic Computer
Week-6	Microprogrammed Control
Week-7	Central Processing Unit
Week-8	Pipeline and Vector Processing
Week-9	Computer Arithmetic
Week-10	Input-Output Organization
Week-11	Memory Organization
Week-12	Multiprocessors

Exam System with Grading

Task	Mark
Final Exam	80%
Lab and Practical Assignments	15%
Tutorials	5%
Total	100%

Mark	Grade
85~100	A+
75~85	A
60~75	B+
50~60	B
<50	F

Lecture-1



Introduction to Computer System Architecture

Lecture-1

Introduction to Computer System Architecture

- What is digital computer?
- Boolean Algebra
- Combinational Circuits
- Flip Flops
- Sequential Circuits
- Integrated Circuits
- Memory Unit

What is a Digital Computer?

What is digital computer?

- A **digital computer** is a digital system that performs various computational tasks.
- It is subdivided into
 - Hardware
 - Main Unit
 - Peripherals
 - Software
 - Operating system (also called **System Programs**)
 - Application programs

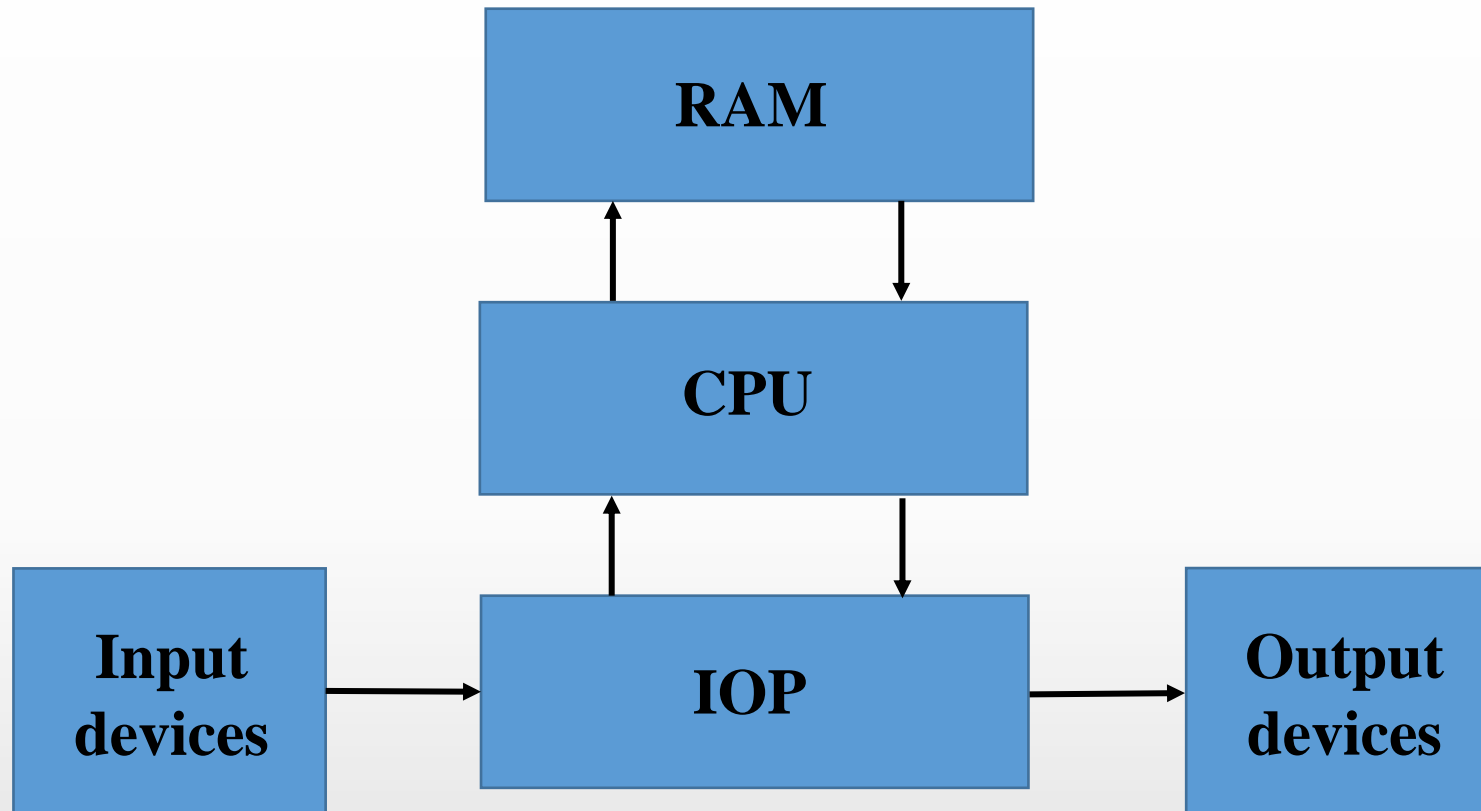


Fig: Block Diagram of a Digital Computer

Boolean Algebra

Boolean Algebra

- A **Boolean algebra** is an algebra that deals with binary variables and logic operations.
- A **Boolean function** can be expressed algebraically with binary variables, the logic operation symbols, parentheses, and equal sign.
- A **truth table** represents the relationship between a function and its binary variables.
- A Boolean function can be transformed from an algebraic expression into a **logic diagram** composed of AND, OR and inverter gates.
- The purpose of Boolean algebra is to facilitate the analysis and design of digital circuits.
- It provides a convenient tool to:
 1. Express in algebraic form a truth table relationship between binary variables.
 2. Express in algebraic form the input-output relationship of logic diagrams.
 3. Find simpler circuits for the same function.


TABLE: Basic Identities of Boolean Algebra

(1) $x + 0 = x$	(2) $x \cdot 0 = 0$
(3) $x + 1 = 1$	(4) $x \cdot 1 = x$
(5) $x + x = x$	(6) $x \cdot x = x$
(7) $x + x' = 1$	(8) $x \cdot x' = 0$
(9) $x + y = y + x$	(10) $xy = yx$
(11) $x + (y + z) = (x + y) + z$	(12) $x(yz) = (xy)z$
(13) $x(y + z) = xy + xz$	(14) $x + yz = (x + y)(x + z)$
(15) $(x + y)' = x'y'$	(16) $(xy)' = x' + y'$
(17) $(x')' = x$	

- To see how the Boolean algebra manipulation is used to simplify digital circuits in order to reduce the logic gates requirements, the following equation can be studied as example.

$$\begin{aligned} F &= ABC + AB\bar{C} + \bar{A}C \\ &= AB(C + \bar{C}) + \bar{A}C \\ &= AB + \bar{A}C \end{aligned}$$

For $F = ABC + AB\bar{C} + \bar{A}C$

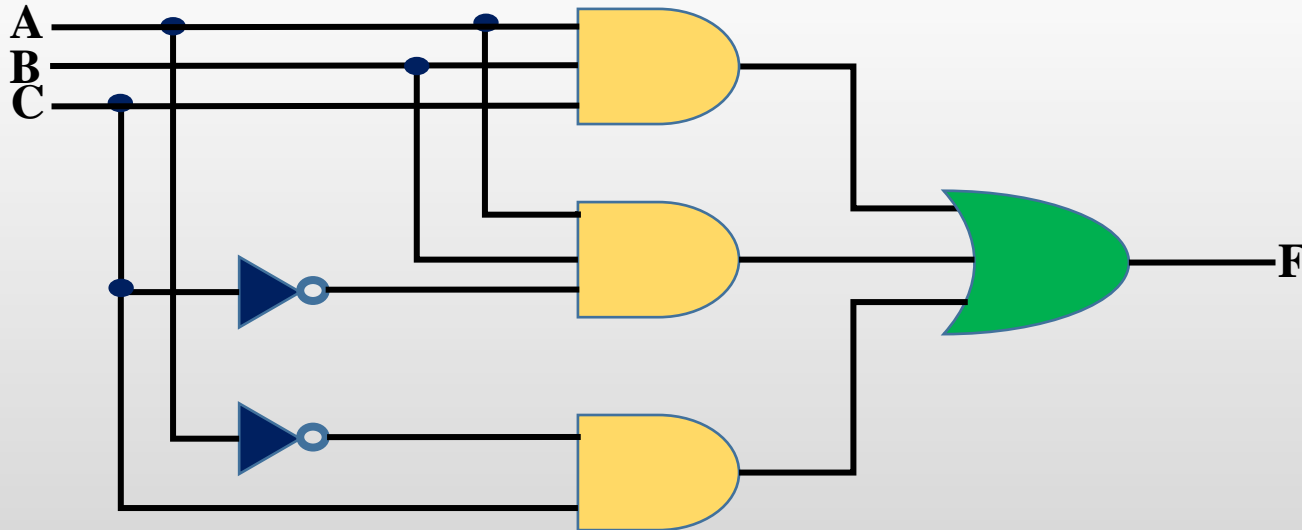

For $F = AB + \bar{A}C$

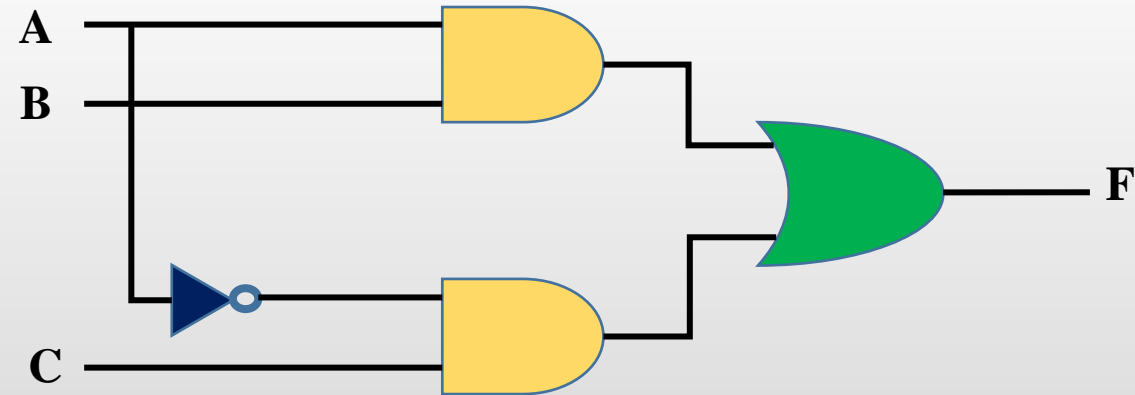


Fig: Two Logic Diagrams for Same Boolean Function

Combinational Circuits

Combinational Circuits

- A **combinational circuits** is a connected arrangement of logic gates with a set of inputs and outputs.
- The procedure to design the combinational circuits involves the following steps.
 - The problem is stated.
 - The input and output variables are assigned letter symbols.
 - The truth table that defines the relationship between inputs and outputs is derived.
 - The simplified Boolean functions for each output are obtained.
 - The logic diagram is drawn.



Fig: Block Diagram of a Combinational Circuit

Adders

- Adders are one kind of combinational circuits.
- An adder is a digital circuit that performs addition of binary numbers.
- Two kinds of adders
 - Half adder
 - Full adder.

For Half adder:


Truth table

A	B	S	C _{in}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

Equation

$$S = \bar{A}B + A\bar{B} = A \oplus B$$
$$C = AB$$

Logic diagram

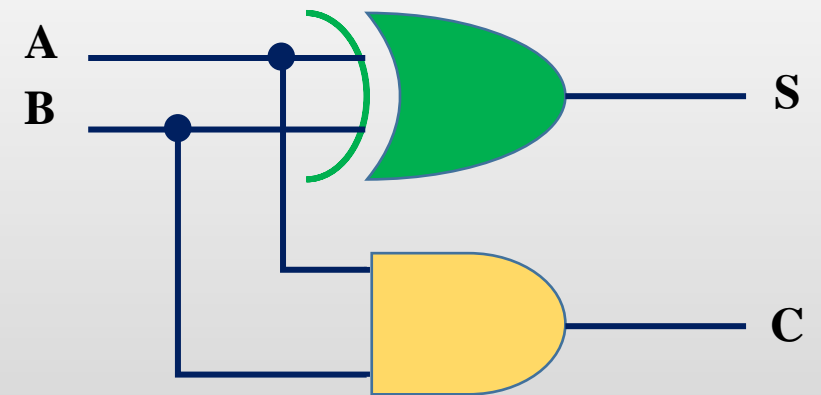

For Full adder:


Truth table

A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Equation

$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = AB + (A \oplus B)C_{in}$$

Logic diagram

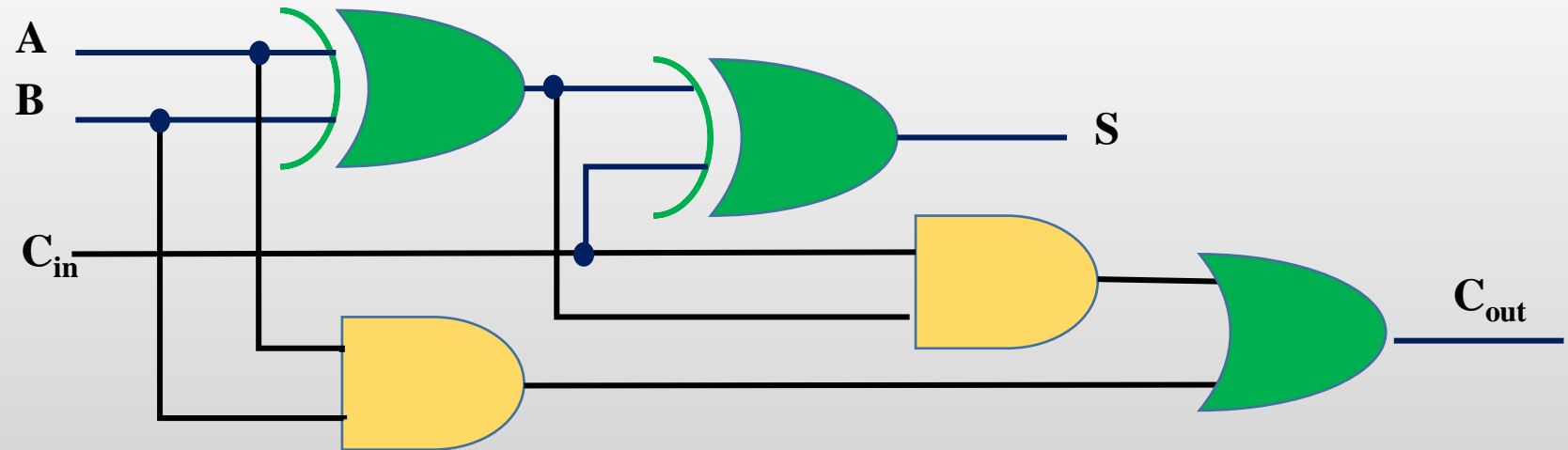

Decoders


- A **decoder** is a combinational circuit that converts binary information from the n coded inputs to a maximum of 2^n unique outputs.

For 3-to-8-line Decoder:

Truth table

Enable	Inputs			Outputs							
E	A2	A1	A0	D7	D6	D5	D4	D3	D2	D1	D0
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

Gate level illustration

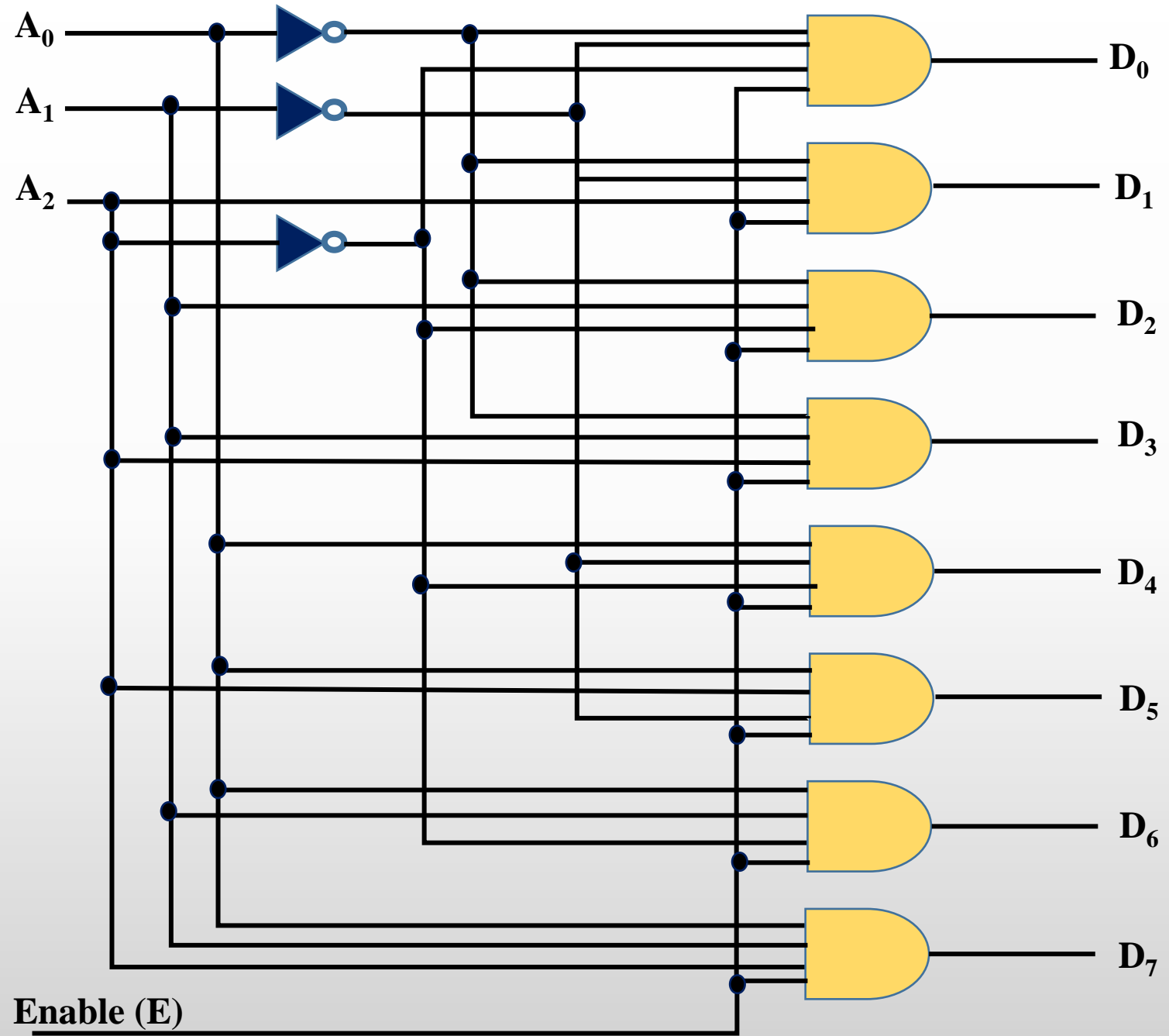

NAND Gate Decoders


- A **decoder** constructed with NAND instead of AND is called NAND gate decoder which becomes more economical to generate the decoder outputs in their complement form.

For 2-to-4-line Decoder with nand gate:

Truth table

E	A1	A0	D0	D1	D2	D3
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	x	x	1	1	1	1

Gate level illustration

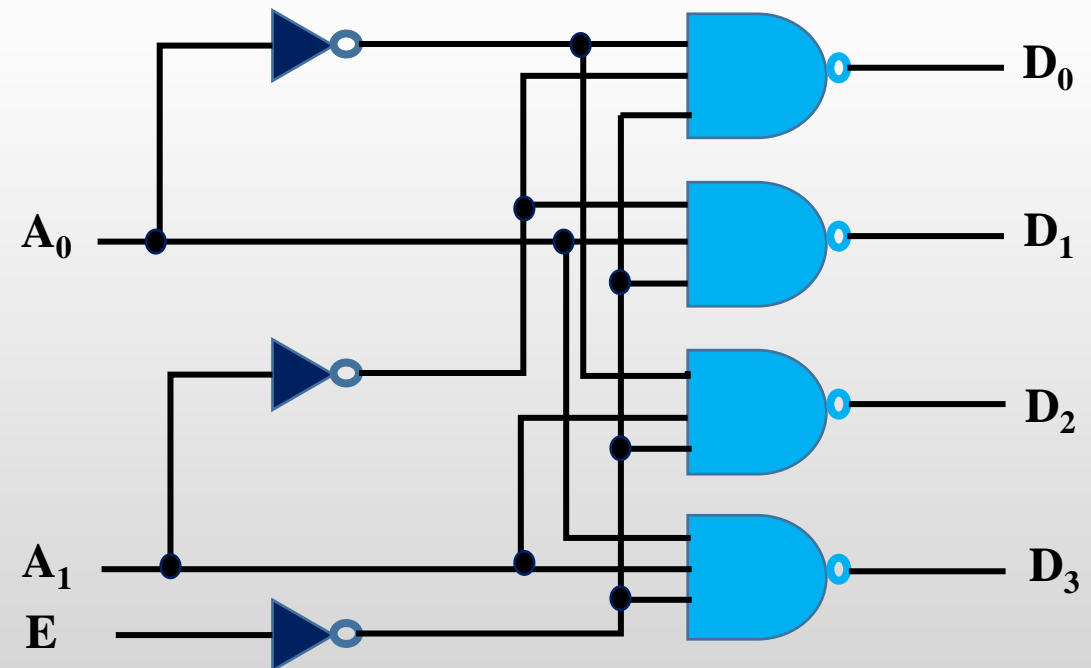

Multiplexer

- A **multiplexer** is a combinational circuit that receives binary information from one of two input data lines and directs it to a single output line.
- The selection of a particular input data line for the output is determined by a set of selection inputs.


For 4 x 1 multiplexer,

$$Y = \overline{S_1}\overline{S_0}I_0 + \overline{S_1}S_0I_1 + S_1\overline{S_0}I_2 + S_1S_0I_3$$


Truth table

Select line		Output
S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

Block diagram

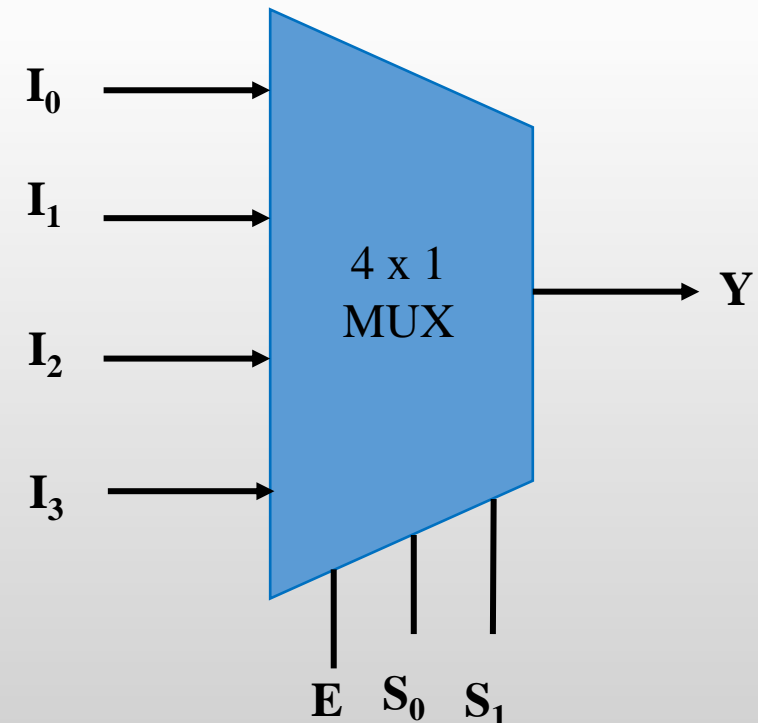

Gate level illustration

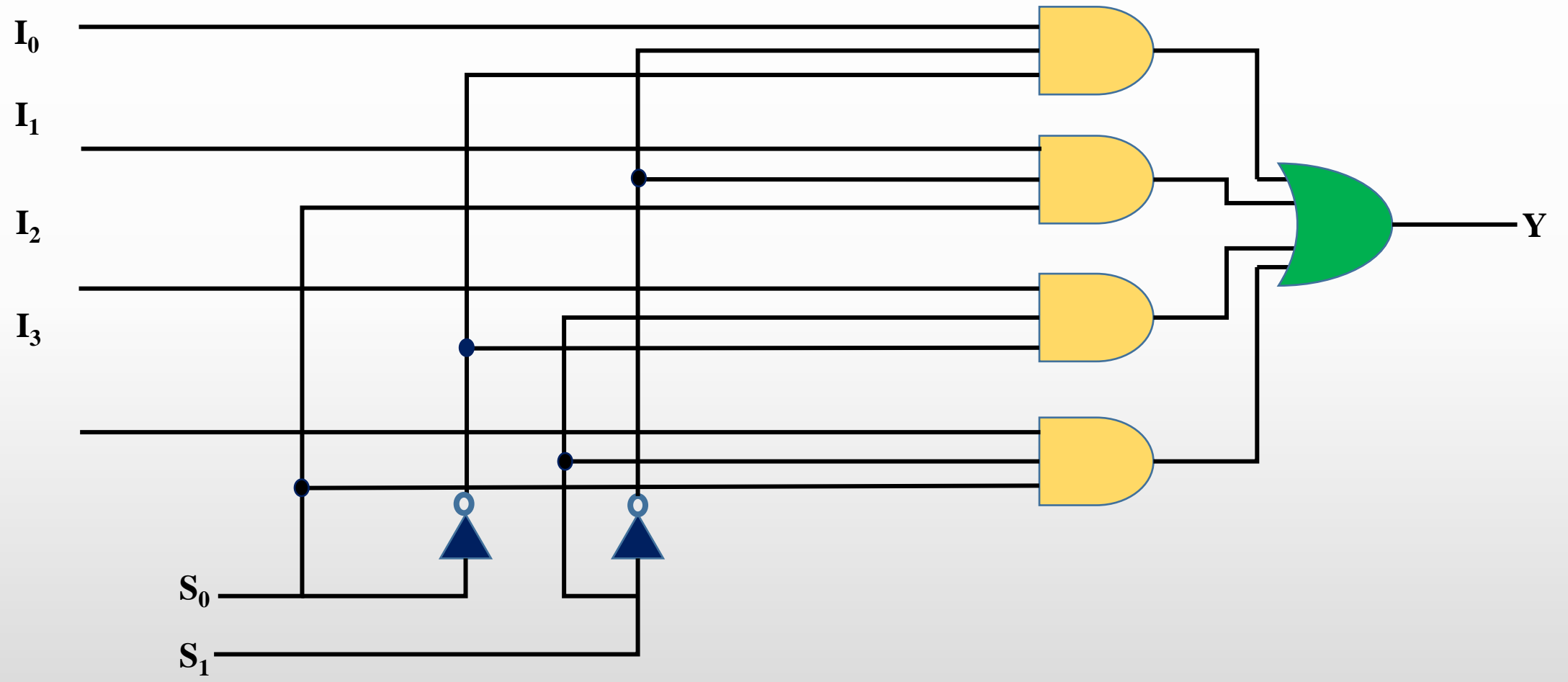

Flip Flops

Flip-flops

- A **flip-flop** is a device that is used to store one single bit of information.
- A flip-flop maintains a binary state until directed by a clock pulse to switch states.
- Different types of flip-flops are
 - SR flip-flop
 - D flip-flop
 - JK flip-flop
 - T flip-flop
- The **difference** among various types of flip-flops is in the number of inputs they possess and in the manner in which the inputs affect the binary state.


SR Flip-flop

- In **SR flip-flop**, two inputs called S (Set) and R (Reset) and one clock called C control the output of this flip-flop according to the values of these input.

Truth table

S	R	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	?

Block Diagram

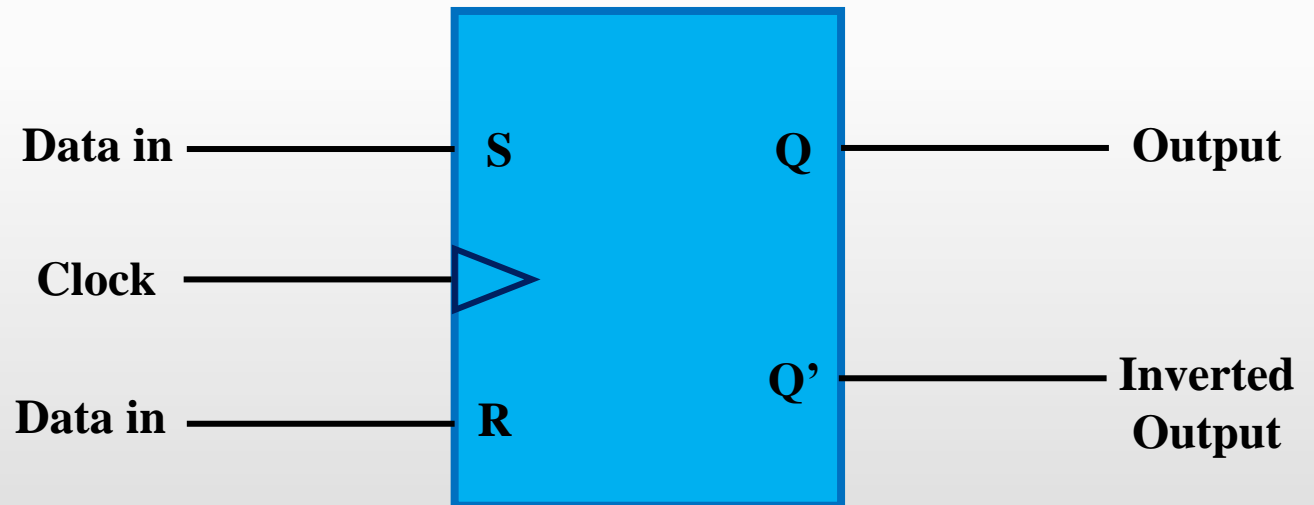


D Flip-flop

- The **D(data) flip-flop** is a slight modification of SR flip-flop by inserting an inverter between S and R and assigning the symbol D to the single input.


Truth table

Clk	Q(t)	D	Q(t+1)
0	x	x	Q(t)
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Block Diagram

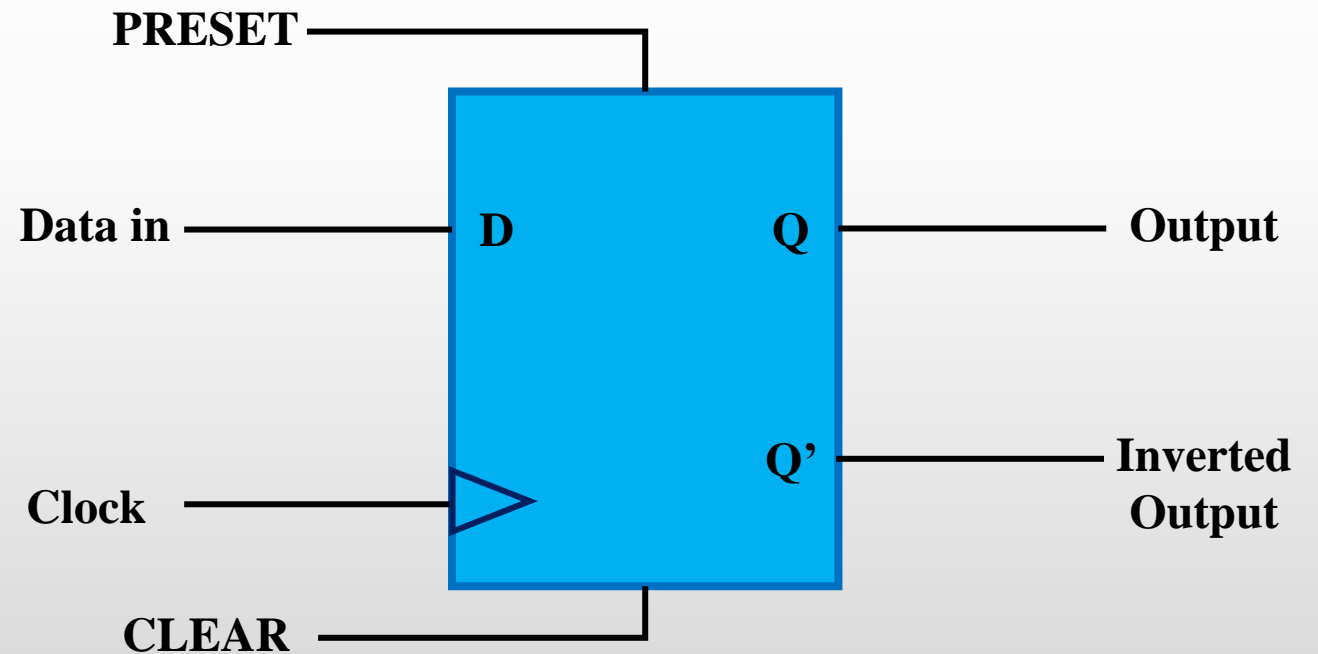

Gate level Illustration of D Flip-flop

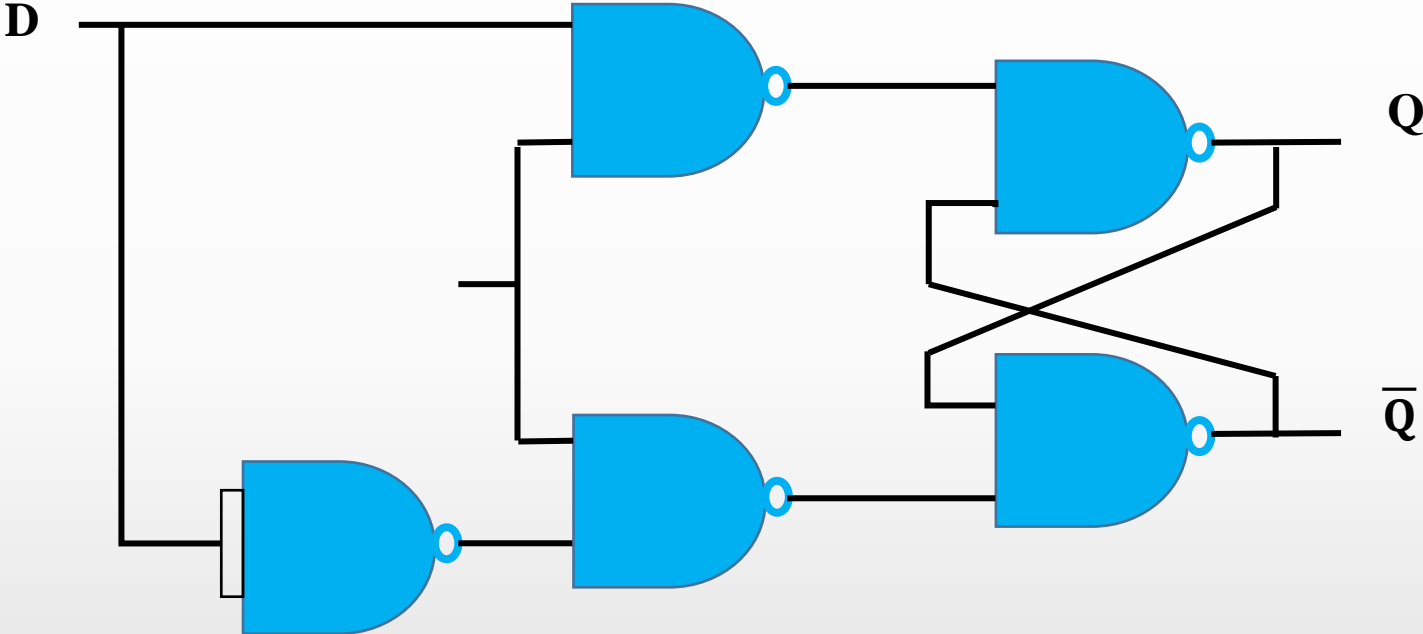


JK Flip-flop

- The **JK flip-flop** is a refinement of SR flip-flop in that the indeterminate condition of SR flip-flop is defined in the JK type.

Truth table

J	K	Q(t+1)	
0	0	Q(t)	No change
0	1	0	Clear to 0
1	0	1	Set to 1
1	1	Q'(t)	Complement

Block Diagram

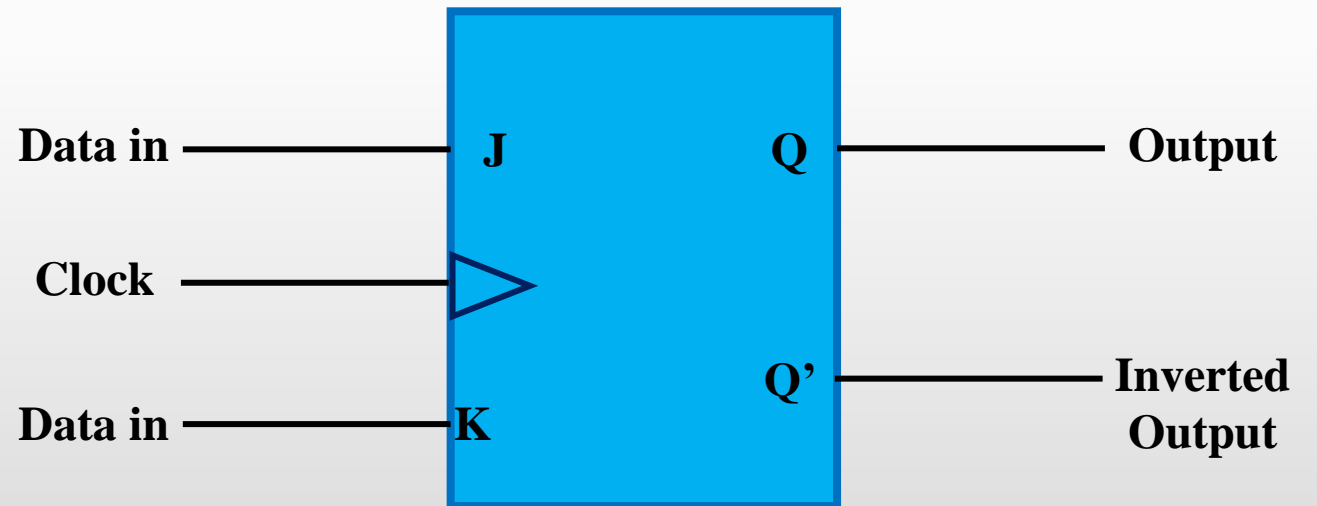


T Flip-flop

- The **T(toggle) flip-flop** is obtained from JK flip-flop in which inputs J and K are connected to provide a single input designated by T.

Truth table

T	Q(t+1)
0	Q(t) No change
1	Q'(t) Complement

Block Diagram

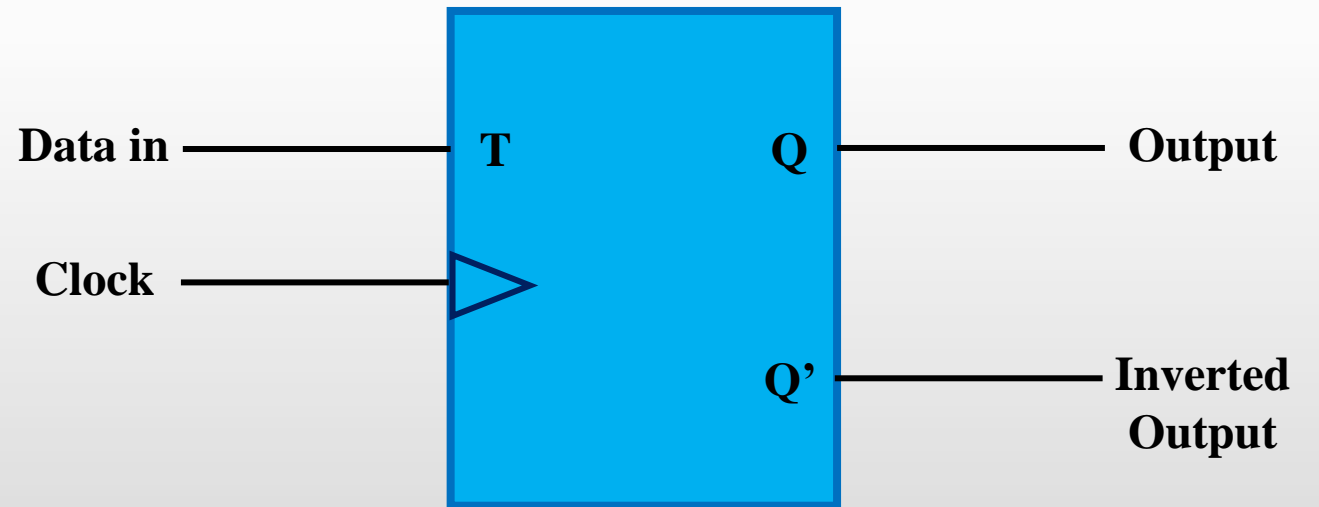

Sequential Circuits

Sequential Circuits

- A **sequential circuit** is an interconnection of flip flops and gates.

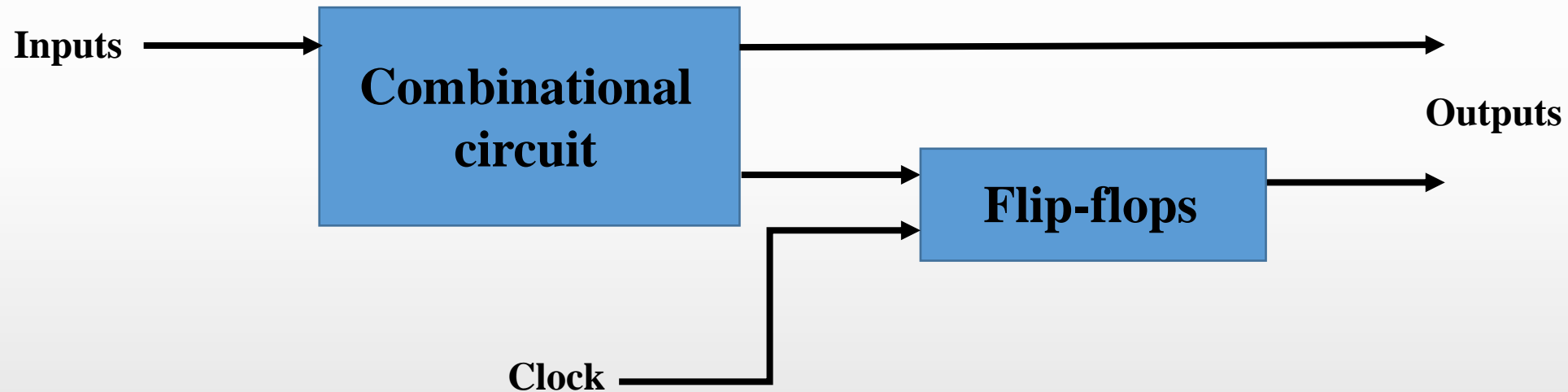


Fig: Block Diagram of a Sequential Circuit


State Table and Diagram of Sequential Circuits

- The **behavior** of a sequential circuit is determined from the inputs, outputs, and the state of its flip flops.
- The state table of this circuit consists of **four** sections, present state, input, next state, and output.
- The **present-state** section shows the states of flip flops A and B at any given time t .
- The **input** section gives the values of x for each possible present state.
- The **next-state** section shows the states of the flip flops one clock period later at time $t+1$.
- The **output** section gives the value of y for each present state and input condition.
- The information available in the state table can be presented graphically in a state diagram.
- In this type of diagram, a state is represented by a circle, and the transition between states is indicated by directed lines connecting the circles.

State Table

Present state		Input	Next state		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

State Diagram

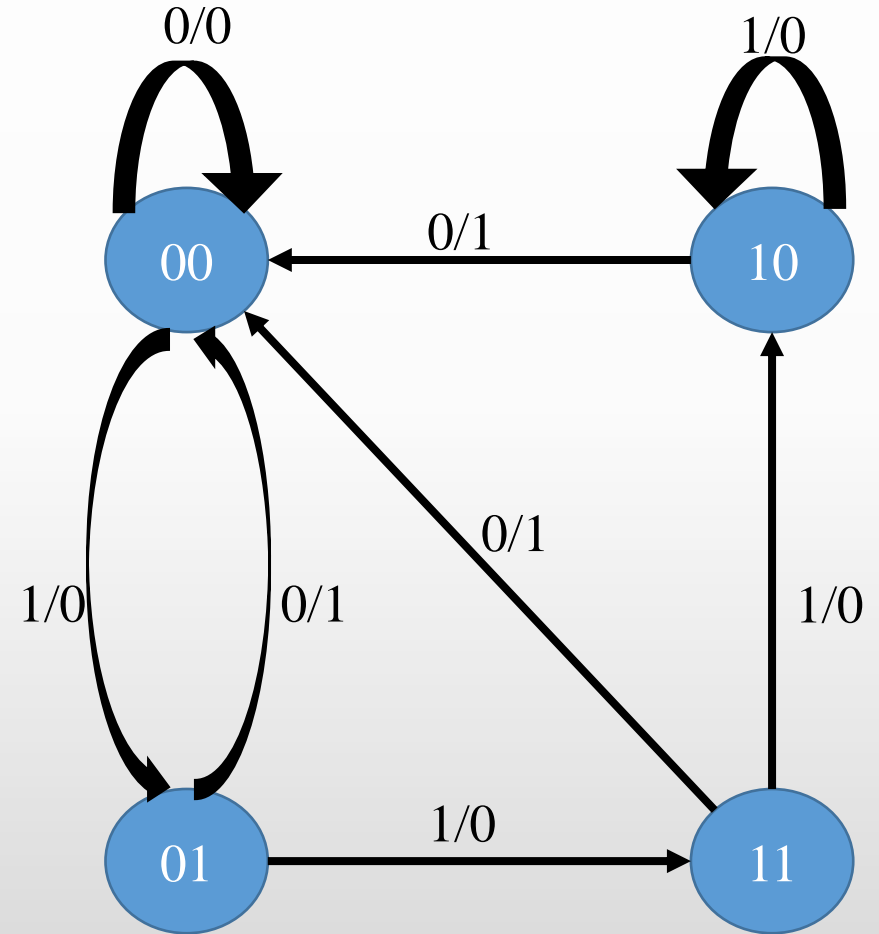

Integrated Circuits

Integrated Circuit

An **integrated circuit** is a small silicon semiconductor crystal, called a chip, containing the electronic components for the digital gates.

- The followings are types of integrated circuits.
 - SSI (Small Scale Integration)
 - ❖ less than 10 gates (*eg. Logic gates*)
 - MSI (Medium Scale Integration)
 - ❖ between 10 and 200 gates (*eg. Flip Flops/ Adders/ Counters/...*)
 - LSI (Large Scale Integration)
 - ❖ between 200 to a few thousands of gates (*eg. Programmable Logic Device*)
 - VLSI (Very Large Scale Integration)
 - ❖ between 10,000 to 100,000 gates (*eg. Complex Programmable Logic Device*)
 - ULSI (Ultra Large-Scale Integration)
 - ❖ more than 100,000 gates (*eg. Microprocessors*)




Registers

Registers

- A **register** is a group of flip flops with each flip flop capable of storing one bit of information.
- An n -bit register has a group of n flip flops and capable of storing any binary information of n -bits.
- In addition to flip flops, a register has combinational gates that perform certain **data-processing** task.
- The **transfer of new information** into the register is referred to as **loading** the register.

For 4-bit register:

Block Diagram

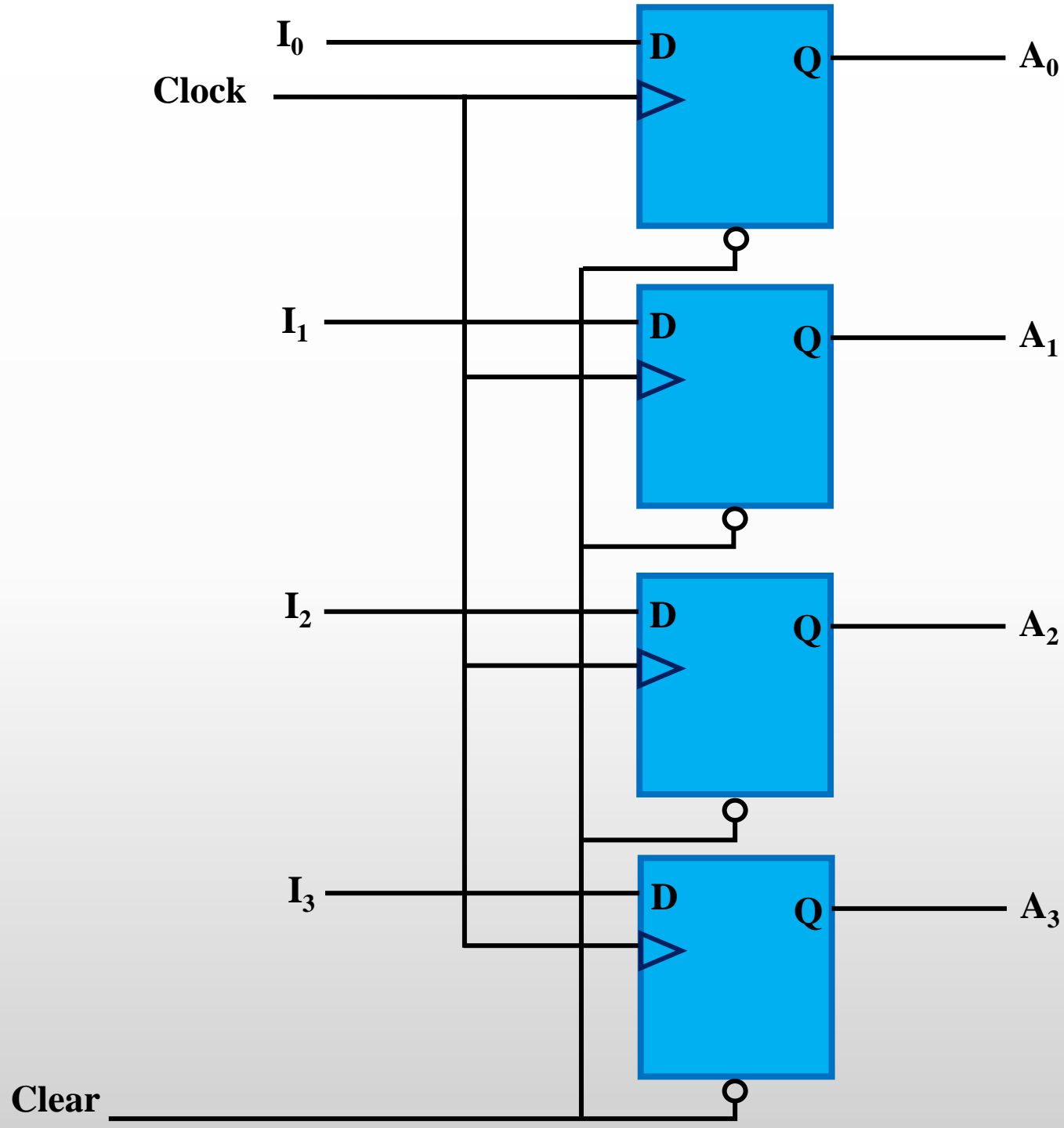


Shift Registers

- A register capable of shifting its binary information in one or both directions is called a **shift register**.
- The **serial input** determines what goes into the leftmost position during the shift.
- The **serial output** is taken from the output of the rightmost flip flop.

For 4-bit register:

Block Diagram

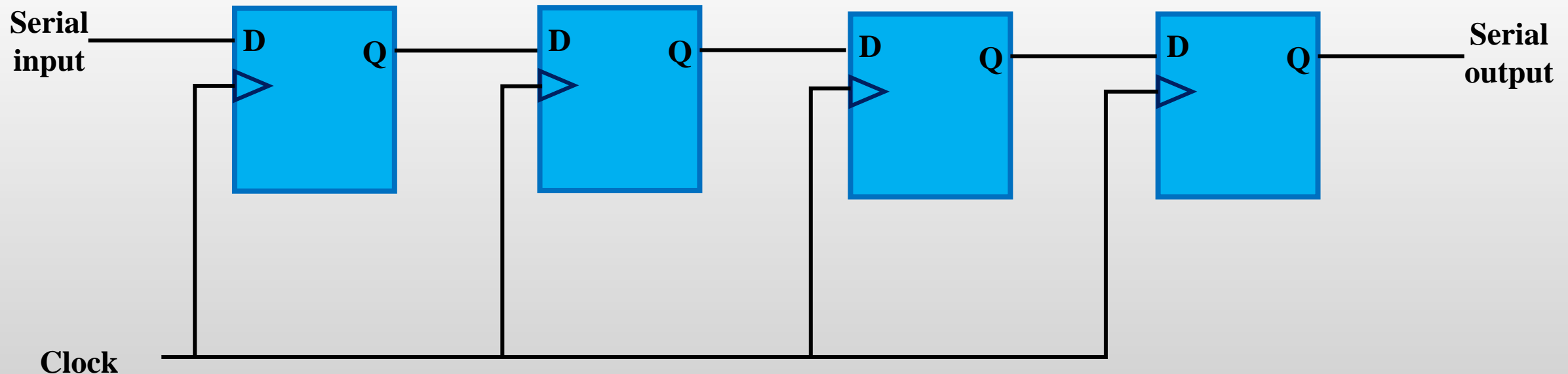

Capabilities of General Shift Register


- The most general shift register has all the **capabilities** listed below.
 1. An input for clock pulses to synchronize all operations.
 2. A shift-right operation and serial input line associated with the shift-right.
 3. A shift-left operation and serial input line associated with the shift-left.
 4. A parallel load operation and n input lines associated with the parallel transfer.
 5. n parallel output lines.
 6. A control state that leaves the information in the register unchanged even though clock pulses are applied continuously.

Binary Counter

Binary Counter

- A **counter** is a register that goes through the predetermined sequence of the stages upon the application of input pulses.
- A **binary counter** is a counter that follows the binary number sequence.
- In addition to flip flops, a register has combinational gates that perform certain data-processing task.
- The **transfer of new information** into the register is referred to as **loading** the register.


Block Diagram

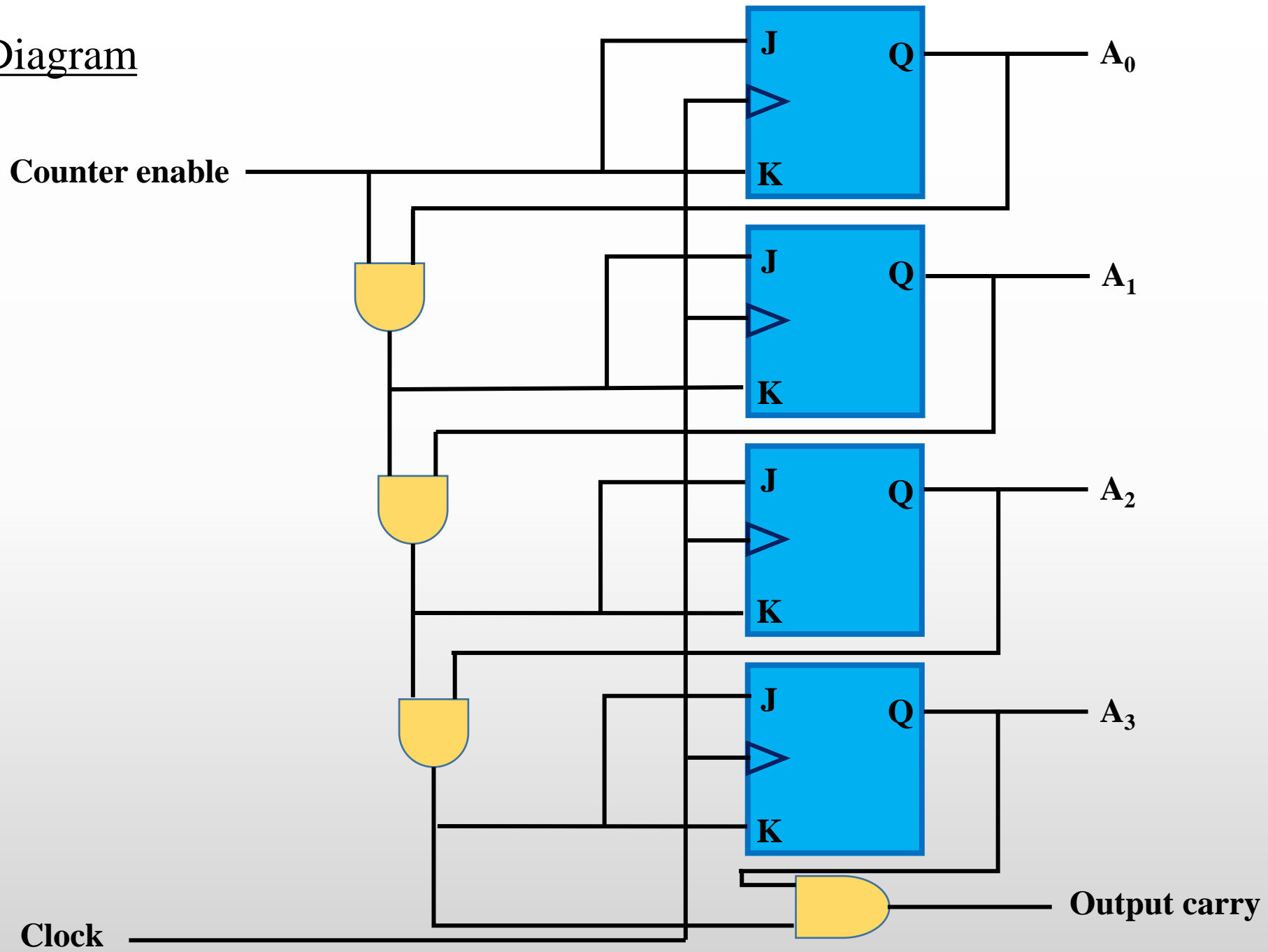

Memory Unit

Memory Unit

- A **memory unit** is a collection of storage cells together with associated circuits needed to transfer information in and out of storage.
- The memory stores binary information in group of bits called **words**.
- A word in memory is an **entity of bits** that in and out of storage as a unit.
- The internal structure of memory unit is specified by the number of words it contains and the number of bits in each word.
- Two major types of memories are used in computer system called random access memory (**RAM**) and read only memory (**ROM**).

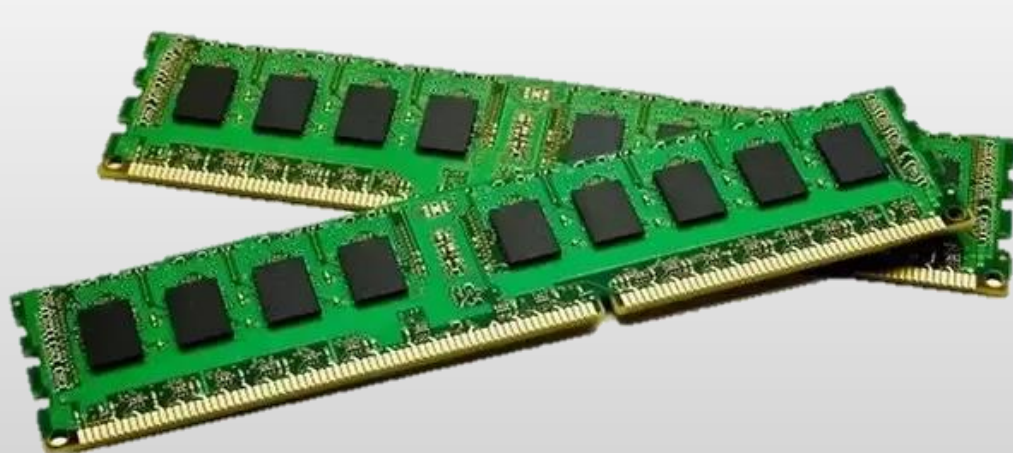


Random Access Memory (RAM)

- In **Random Access Memory (RAM)**, the memory cells can be accessed for information transfer from any desired random location.
- The two operations that a random access memory can perform are **read** and **write** operations.
- The **write** signal specifies a **transfer-in** operation and the **read** signal specifies a **transfer-out** operation.
- The steps of transferring a new word to be stored into memory are as follows.
 - Apply the binary address of the desired word into the address lines.
 - Apply the data bits that must be stored in memory into the data input lines.
 - Activate the write input.
- The steps of transferring a stored word out of memory are as follows.
 - Apply the binary address of the desired word into the address lines.
 - Activate the read input.

Some Features of RAM

- It is used in computer's regular operations, after **loading** the **OS**.
- It is a fast process for writing data.
- It is a type of **volatile** memory, i.e. stored data is lost when powering off.
- It stores quite a lot of data.
- Two types of RAM: **Static** RAM (SRAM) and **Dynamic** RAM (DRAM)

Block Diagram

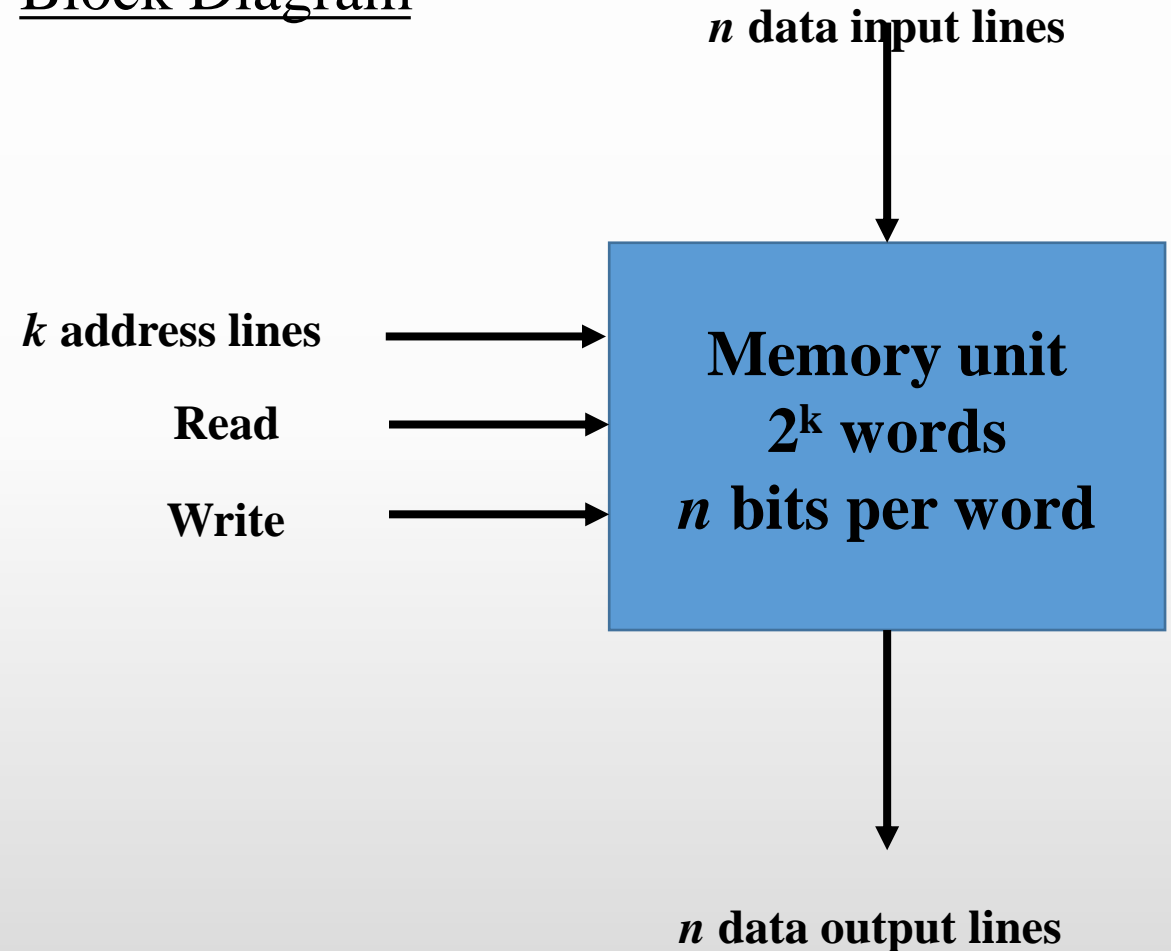

Static RAM (SRAM)

- **Static RAM** is a type of semiconductor random access memory in which each bit of data is stored in the flip-flop.
- It is a **volatile memory** that requires power to maintain the stored data and information.
- It provides **faster access** to data and is more **expensive** than DRAM.
- It is mainly used for the **cache** memory in the computer system.



Dynamic RAM (DRAM)

- **Dynamic RAM** is a type of semiconductor random access memory in which each bit of data is stored in a memory cell.
- It is based on the **metal-oxide-semiconductor** technology.
- It is more **complicated** and **time-consuming** than SRAM, but it is more widely used.
- It is mainly used for the **main memory** and **graphics cards** (graphics memory) in the computer system.



Read Only Memory (ROM)

- A **Read Only Memory** is a memory unit that performs the read operation only; it does not have a write capability.
- A ROM is **restricted** to reading words that are permanently stored within the unit.
- ROM is used for storing **fixed programs** that are not to be altered and the tables of contents that are not to be changed.
- There are different types of ROM used in today computer system.
 - Programmable Read Only Memory (PROM)
 - Erasable PROM (EPROM)
 - Electrically EPROM (EEPROM)

Thank You

Lecture for Next Week



- **Different types of data presentation**
 - **Data types**
 - **Fixed-point presentation**
 - **Floating-point presentation**
 - **Binary codes**
 - **Error detection codes**